

XMUT 101

Engineering Technology

A/Prof. Pawel Dmochowski

School of Engineering and Computer Science
Victoria University of Wellington


Victoria
UNIVERSITY OF WELLINGTON
*Te Whare Wānanga
o te Ūpoko o te Ika a Māui*



CAPITAL CITY UNIVERSITY

What are Logic Gates?

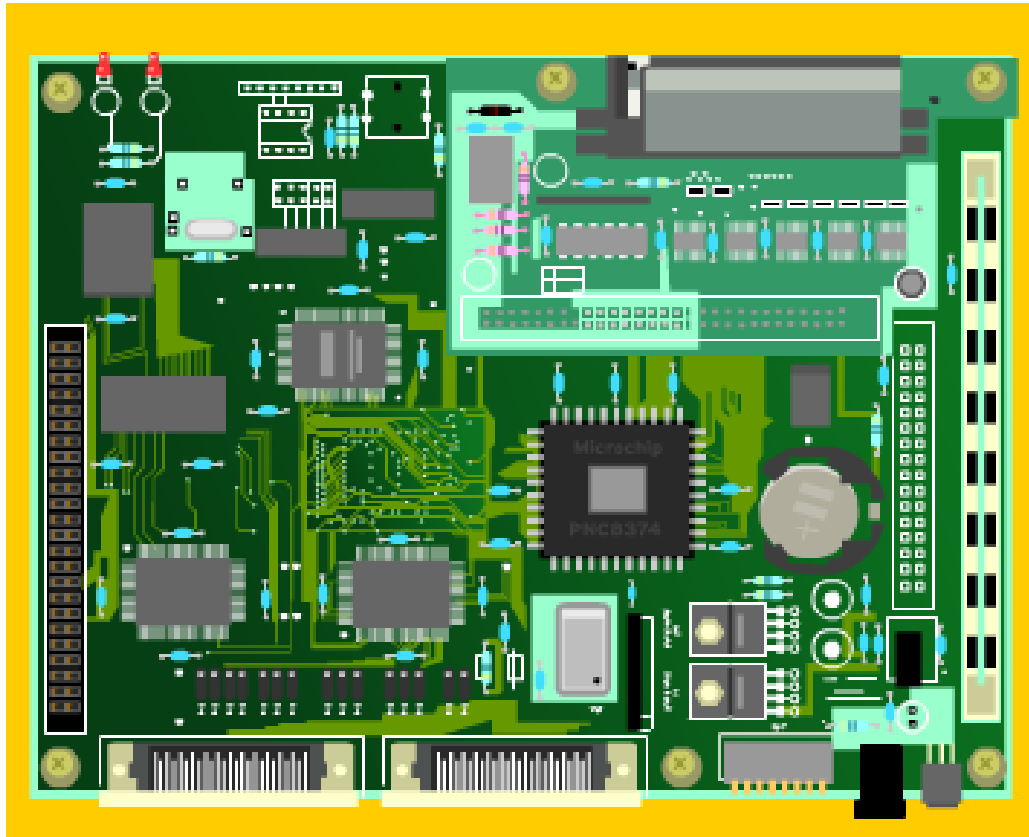
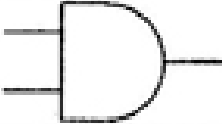
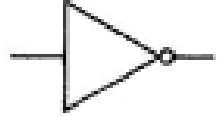
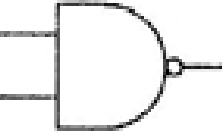



- Basic building blocks of a digital circuit



What are Logic Gates?

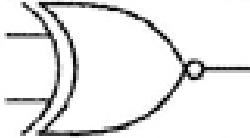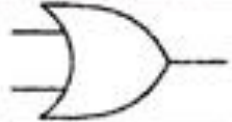
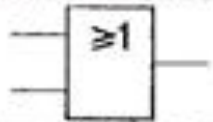
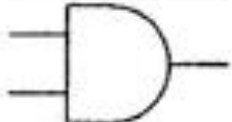
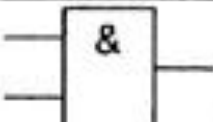
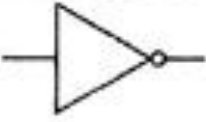
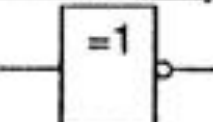

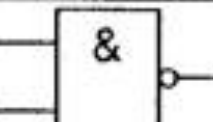

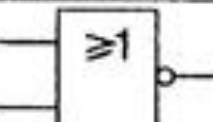

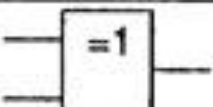

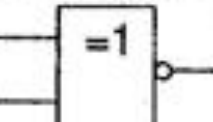
- Basic building blocks of a digital circuit
- Data processing on the circuit is controlled using transistors
- Output depends on the logic gate and the input
- Input is one of two states – high (1) or low (0)
- Output is one of two states – high (1) or low (0)
- There are seven types of logic gates:
 - 3 basic types: AND, OR, NOT
 - NAND, NOR, XOR, XNOR

Logic Gates Symbols

Gate	Symbol
OR	
AND	
NOT	
NAND	
NOR	
EX-OR or X-OR	
EX-NOR or X-NOR	

Logic Gates Symbols


Another symbol

Gate	Symbol	ICE
OR		
AND		
NOT		
NAND		
NOR		
EX-OR or X-OR		
EX-NOR or X-NOR		

Three Basic Logic Gates

1. AND gate
2. OR gate
3. NOT gate (also known as Inverter)

The AND Gate

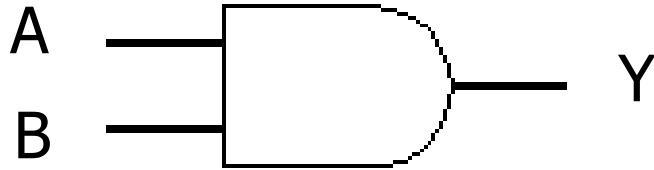


- If both of the 2 input signals are High, the output will also be High.
- If 1 or 2 of the input signals are Low, the output will also be Low.

Truth Tables

- A **truth table** describes (or shows) the relationship between the input(s) and output of a logic circuit.
- The number of entries corresponds to the number of inputs.
 - A 2-inputs table would have $2^2 = 4$ entries.
 - A 3-inputs table would have $2^3 = 8$ entries.
 - A 4-inputs table would have $2^4 = 16$ entries.

The AND Gate

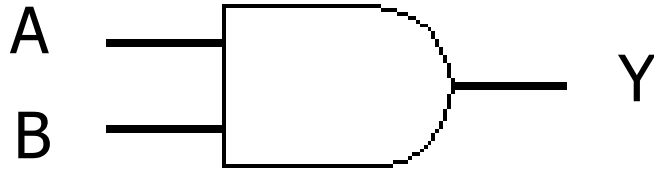


Truth Table

- If the 2 input signals are High, the output will also be High.
- If 1 or 2 of the input signals are Low, the output will also be Low.

Inputs

A	B	Y (Output)
0	0	0
0	1	0
1	0	0
1	1	1

The AND Gate – Exercise

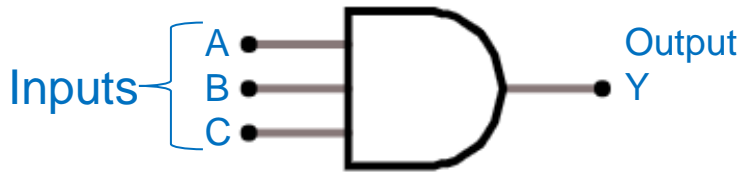


- If the 3 input signals are High, the output will also be High.
- If 1 input signal is Low, the output will also be Low.

Truth Table

Inputs			Y (Output)
A	B	C	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

The OR Gate

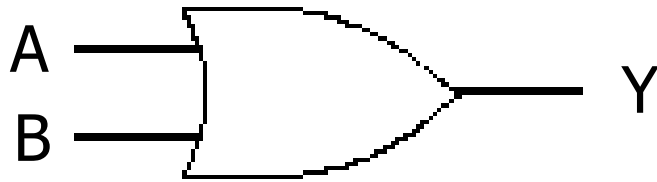


- If either of the two input signals are High (= 1), or both of them are High, the output will be High.

Truth Table

Inputs

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

The OR Gate – Exercise

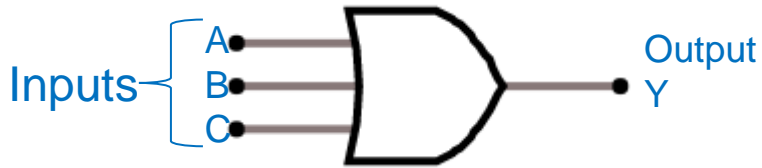

- If at least one of the inputs is High, the output will be High.

Truth Table

Inputs

A	B	C	Y (Output)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

The NOT Gate (also known as the Inverter)



- The output is the opposite of the input signal.


Truth Table

A	Y
0	1
1	0


Describing Circuit Functionality: Waveforms

- Waveforms provide another approach for representing functionality.
- Values are either high (logic 1) or low (logic 0).

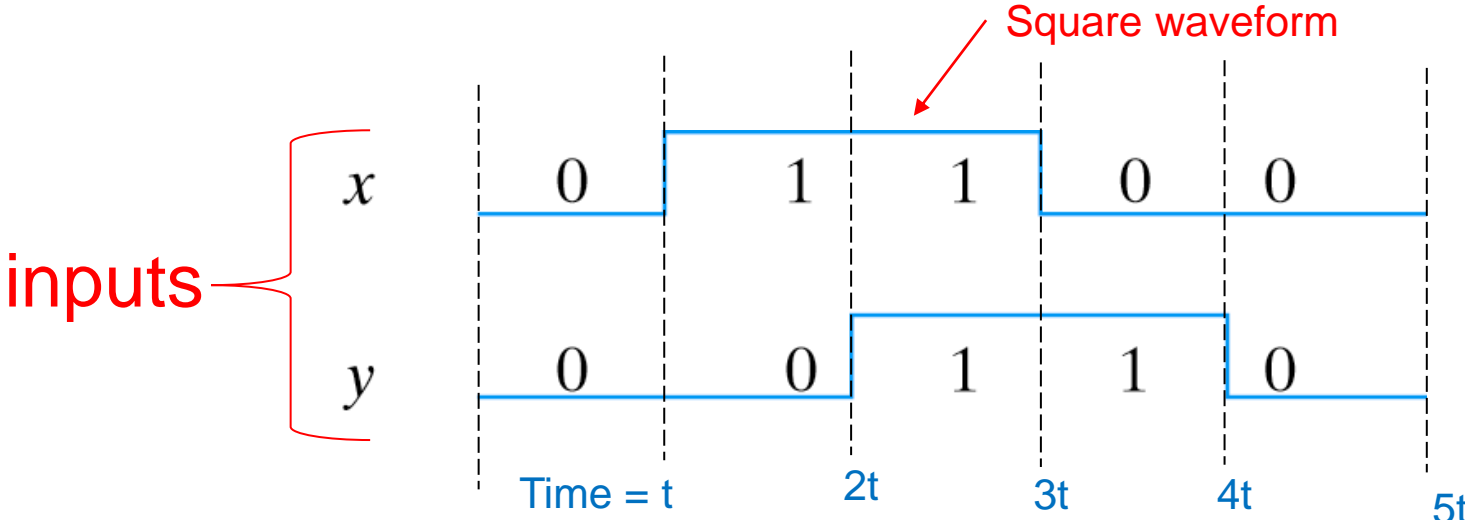
Describing Circuit Functionality: Waveforms



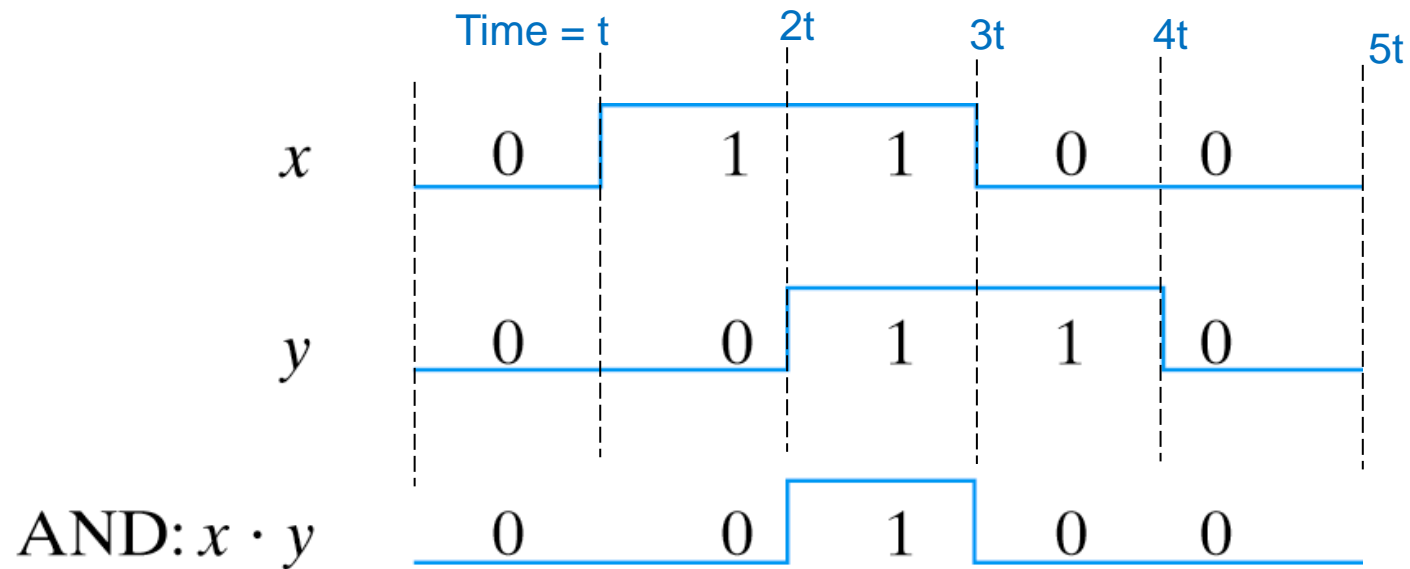
Describing Circuit Functionality: Waveforms



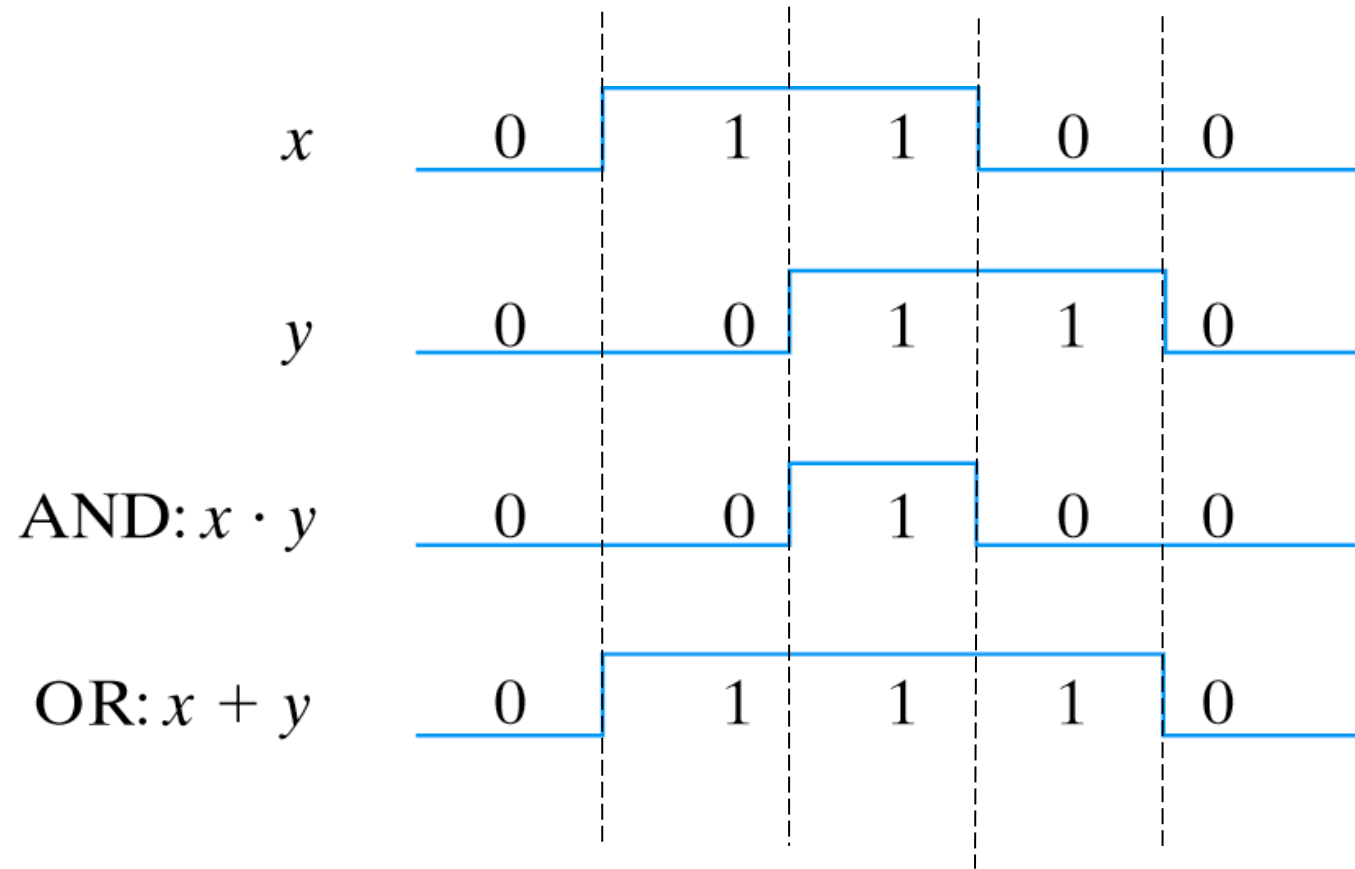Describing Circuit Functionality: Waveforms




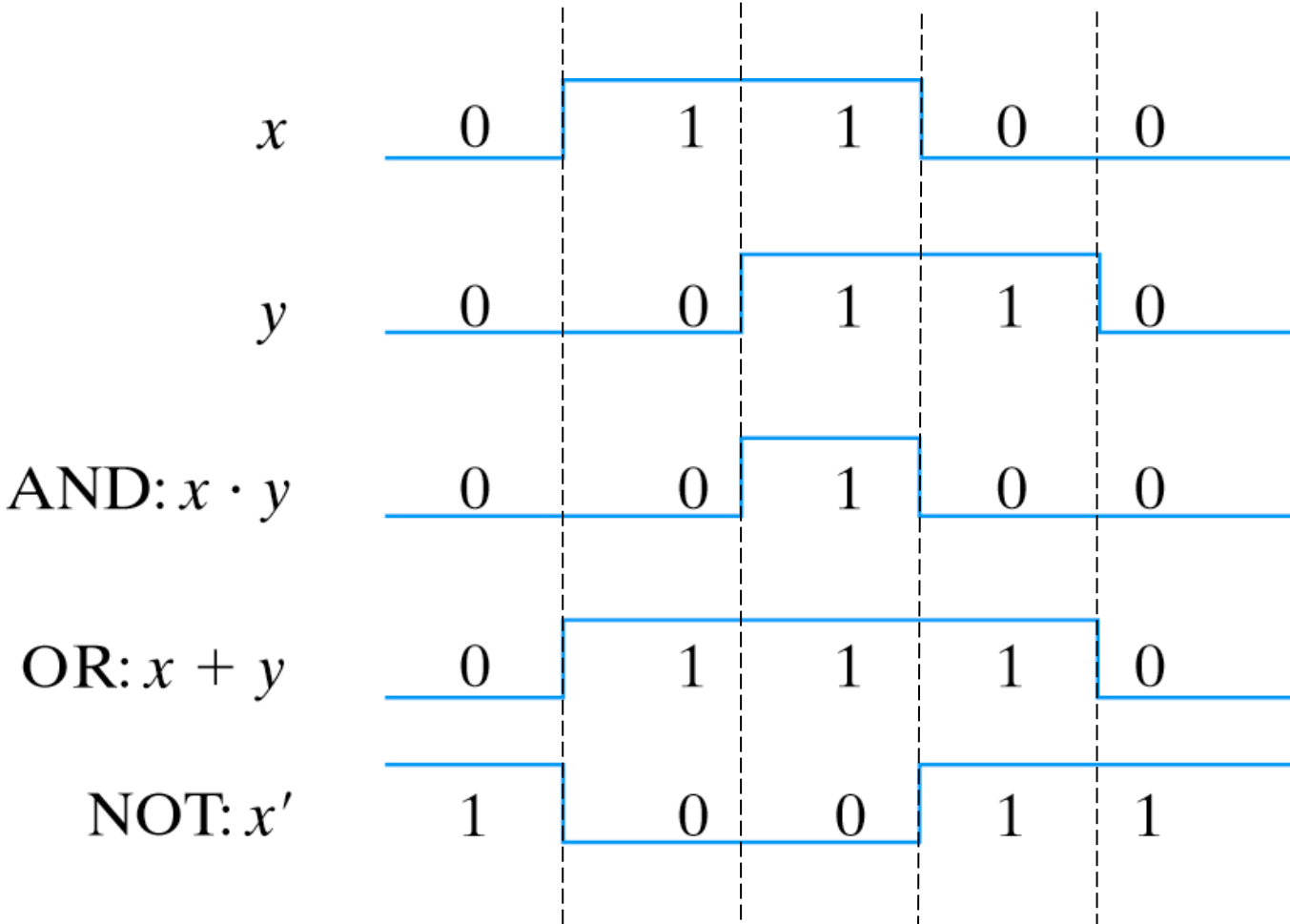Describing Circuit Functionality: Waveforms




Consider three-input gates

3 Inputs OR Gate


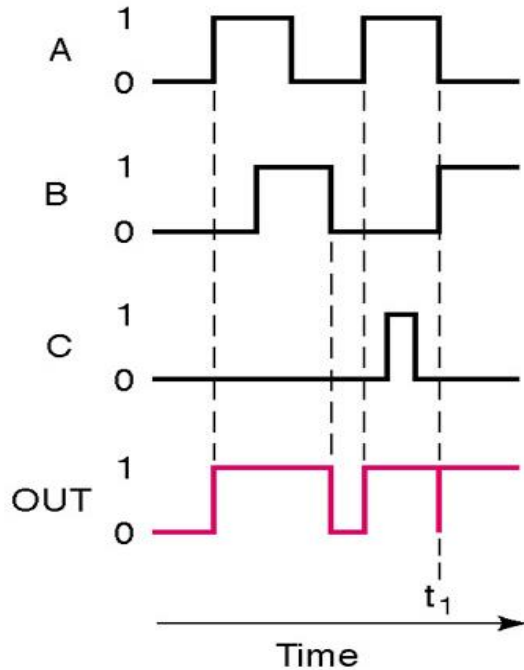


Waveform diagram

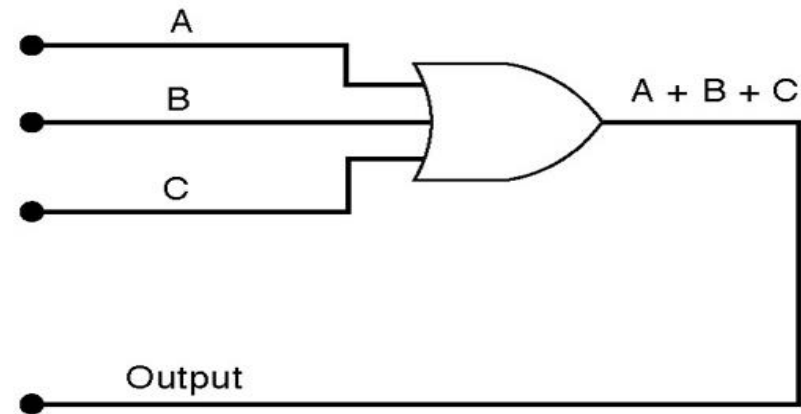

Logic symbol

Consider three-input gates

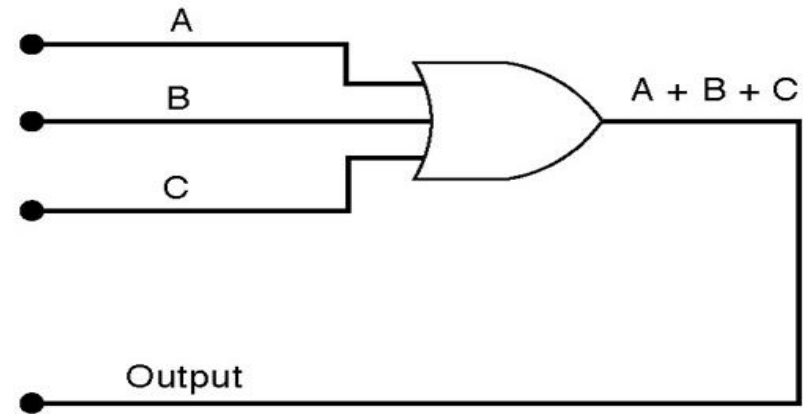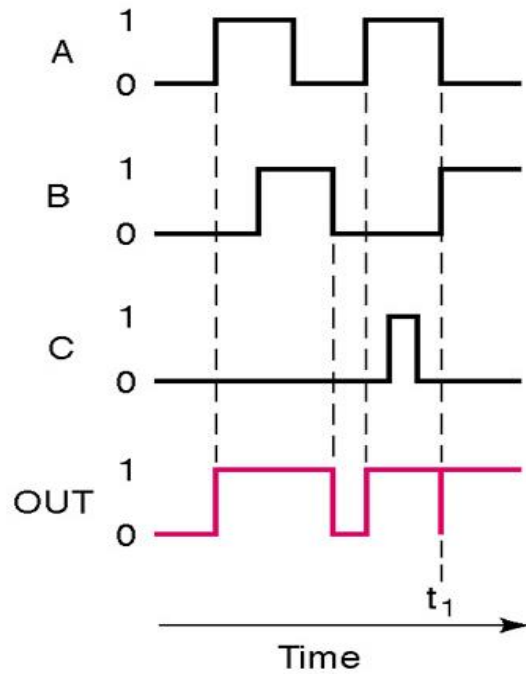


3 Input OR Gate

Truth table

A	B	C	$x = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Consider many inputs!

Inputs		Output
A	B	x
0	0	1
0	1	0
1	0	1
1	1	0

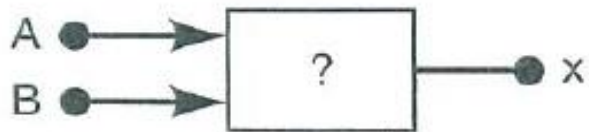


(a)

Consider many inputs!

Inputs		Output
A	B	x
0	0	1
0	1	0
1	0	1
1	1	0

A	B	C	x
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


(b)

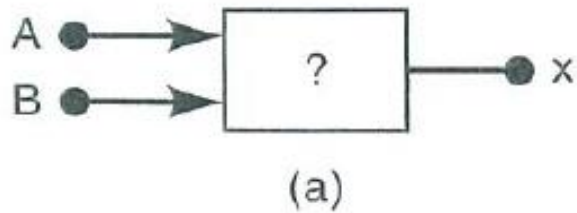

Consider many inputs!

Diagram illustrating a logic block with two inputs (A, B) and one output (x). The inputs are labeled "Inputs" and the output is labeled "Output".

A	B	x
0	0	1
0	1	0
1	0	1
1	1	0

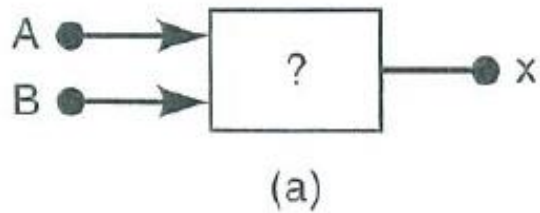

A	B	C	x
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(b)

A	B	C	D	x
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

(c)

Boolean Operators

Summarized rules for OR

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

Boolean Operators

Summarized rules for OR and AND

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

Boolean Operations


Summarized rules for **OR**, **AND** and **NOT**

<i>OR</i>	<i>AND</i>	<i>NOT</i>
$0 + 0 = 0$	$0 \cdot 0 = 0$	$\overline{0} = 1$
$0 + 1 = 1$	$0 \cdot 1 = 0$	$\overline{1} = 0$
$1 + 0 = 1$	$1 \cdot 0 = 0$	
$1 + 1 = 1$	$1 \cdot 1 = 1$	


These three basic Boolean operations can describe any logic circuit.

Describing Logic Circuits Algebraically

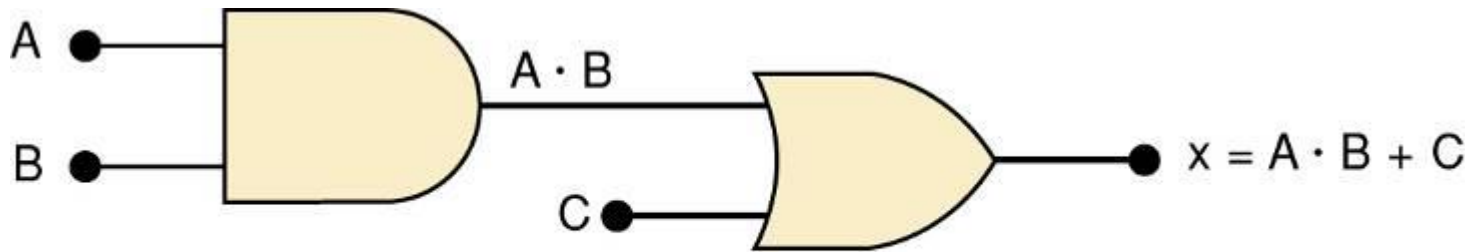- If an expression contains both **AND** and **OR** gates, the **AND** operation will be performed first.




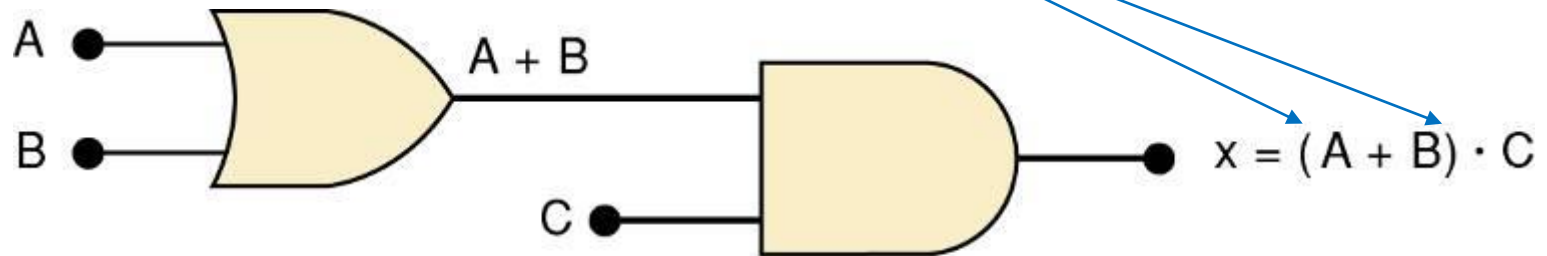- Unless there is a **parenthesis** in the expression.




Describing Logic Circuits Algebraically

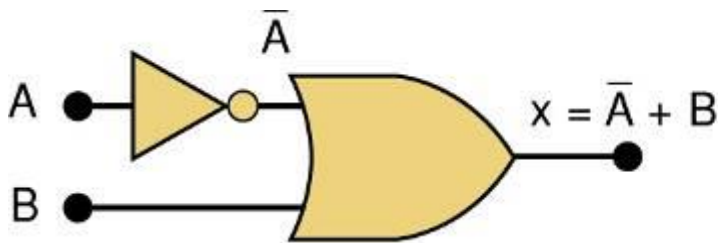- Whenever an INVERTER is present, output is equivalent to input, with a bar over it.
 - Input A through an inverter equals \bar{A} .




(a)

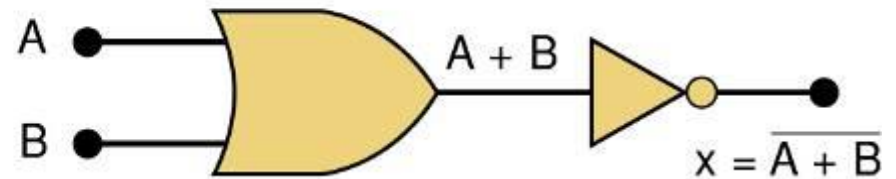

(b)


Describing Logic Circuits Algebraically

Example 1

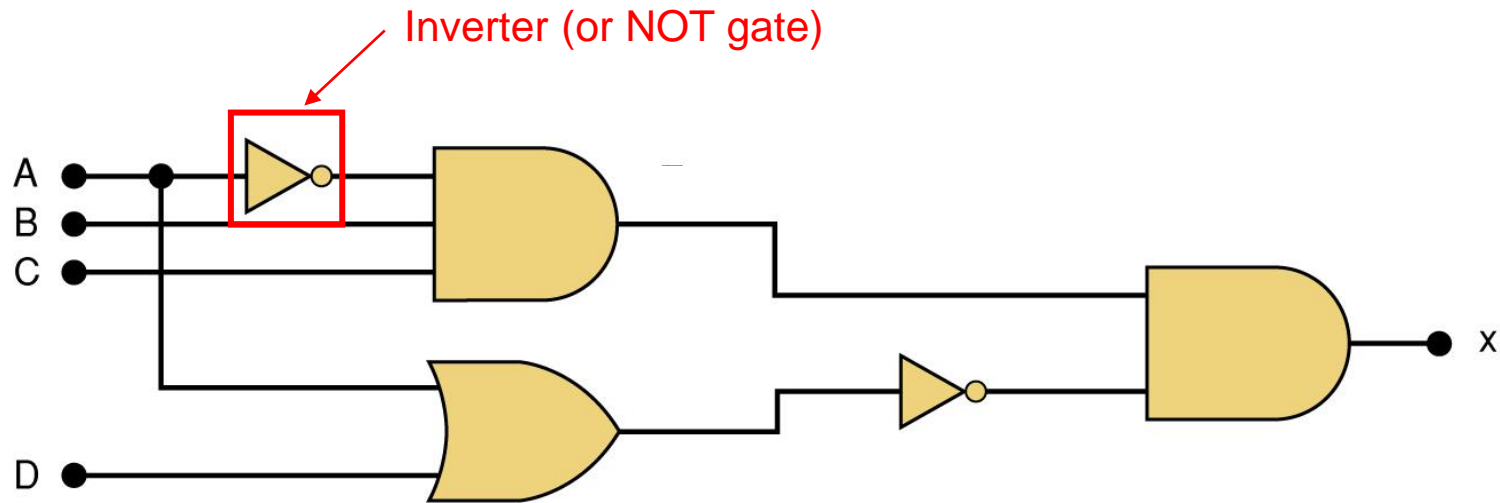


Describing Logic Circuits Algebraically

Example 1

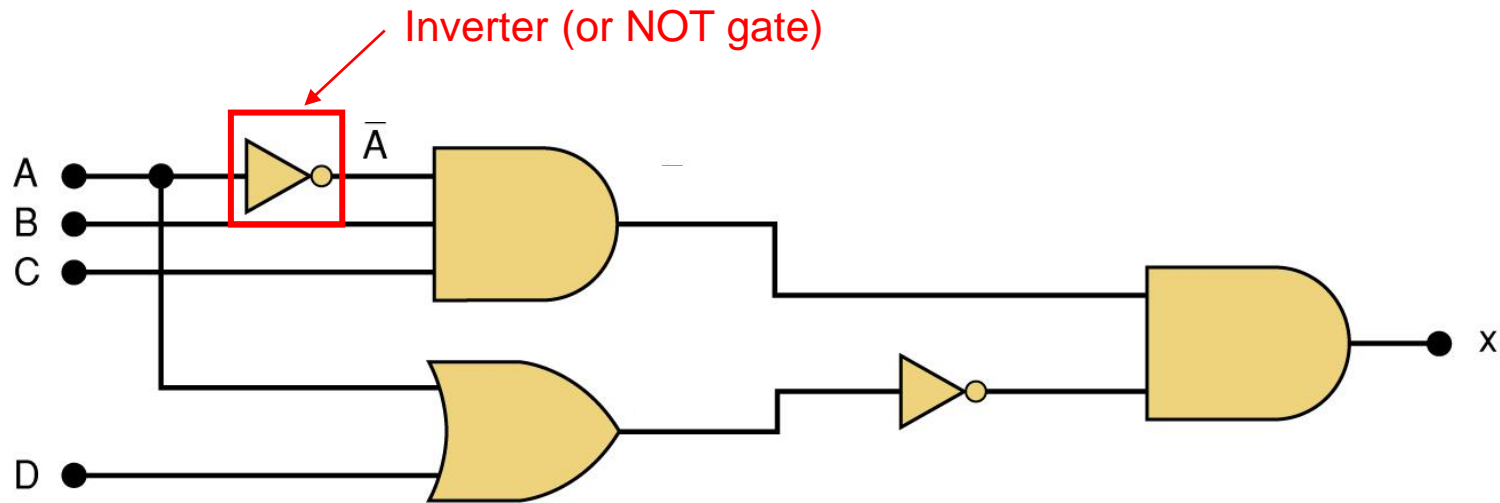


Describing Logic Circuits Algebraically

Example 1

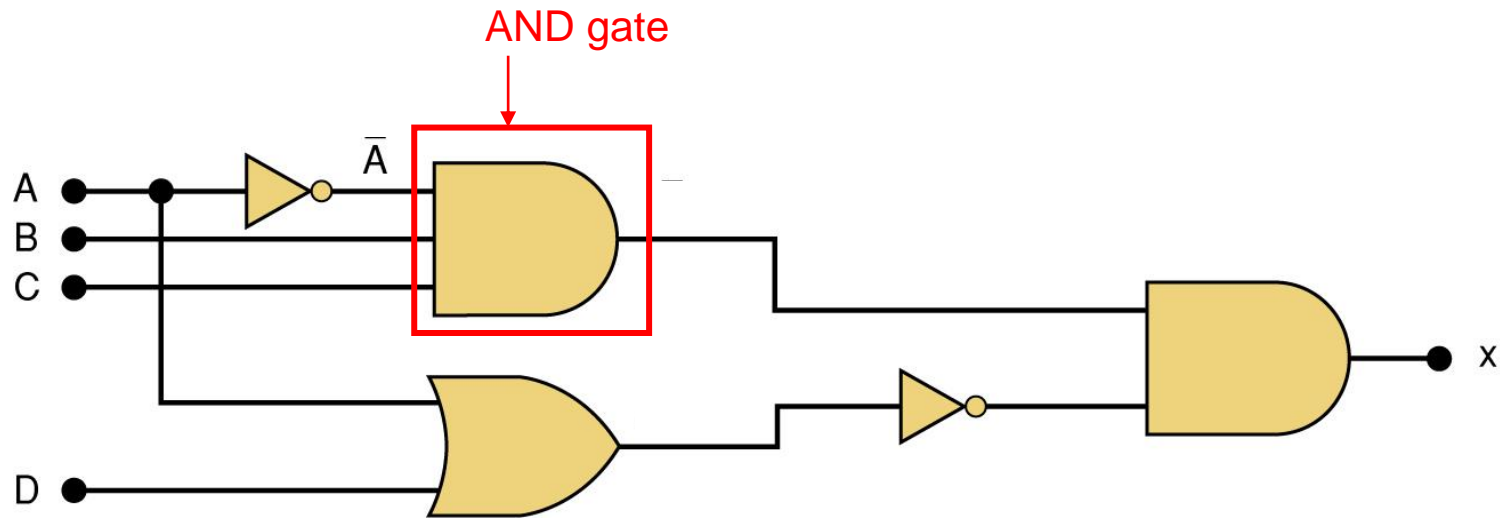


Describing Logic Circuits Algebraically

Example 1

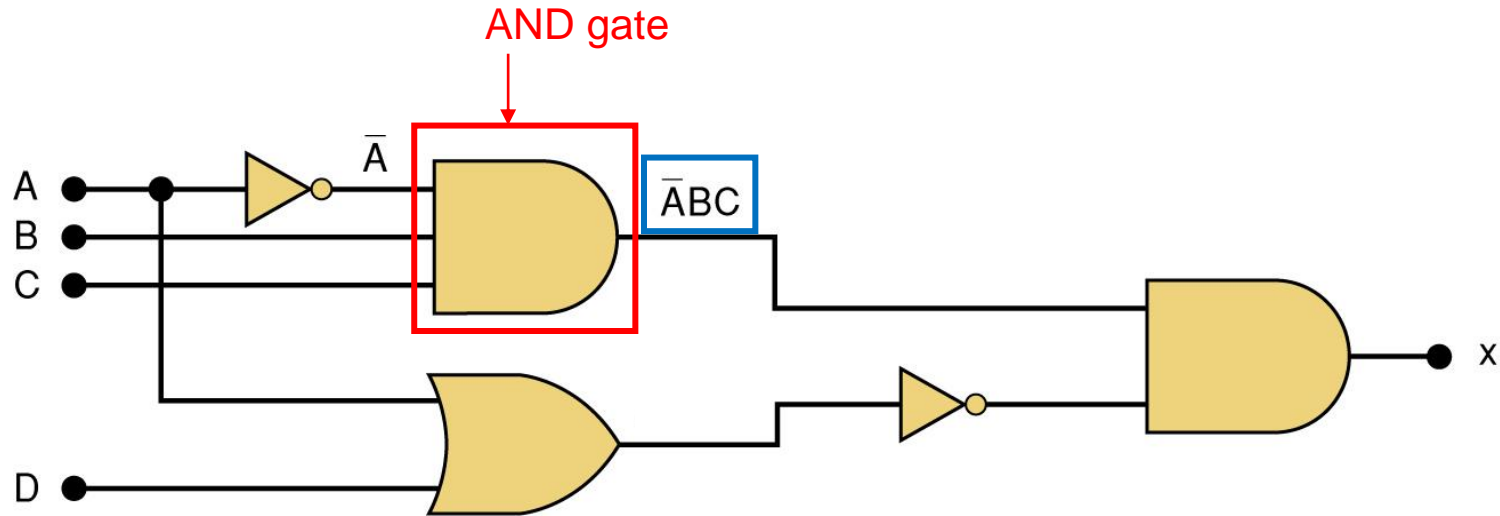


Describing Logic Circuits Algebraically

Example 1

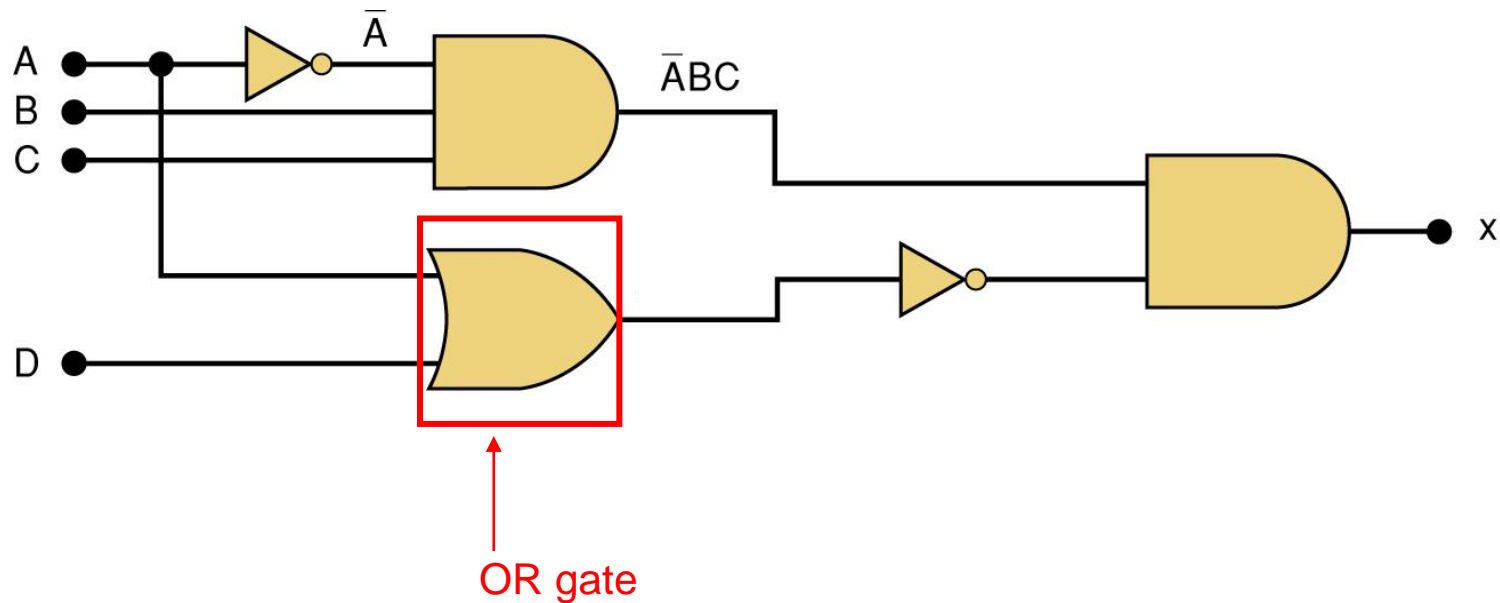


Describing Logic Circuits Algebraically

Example 1

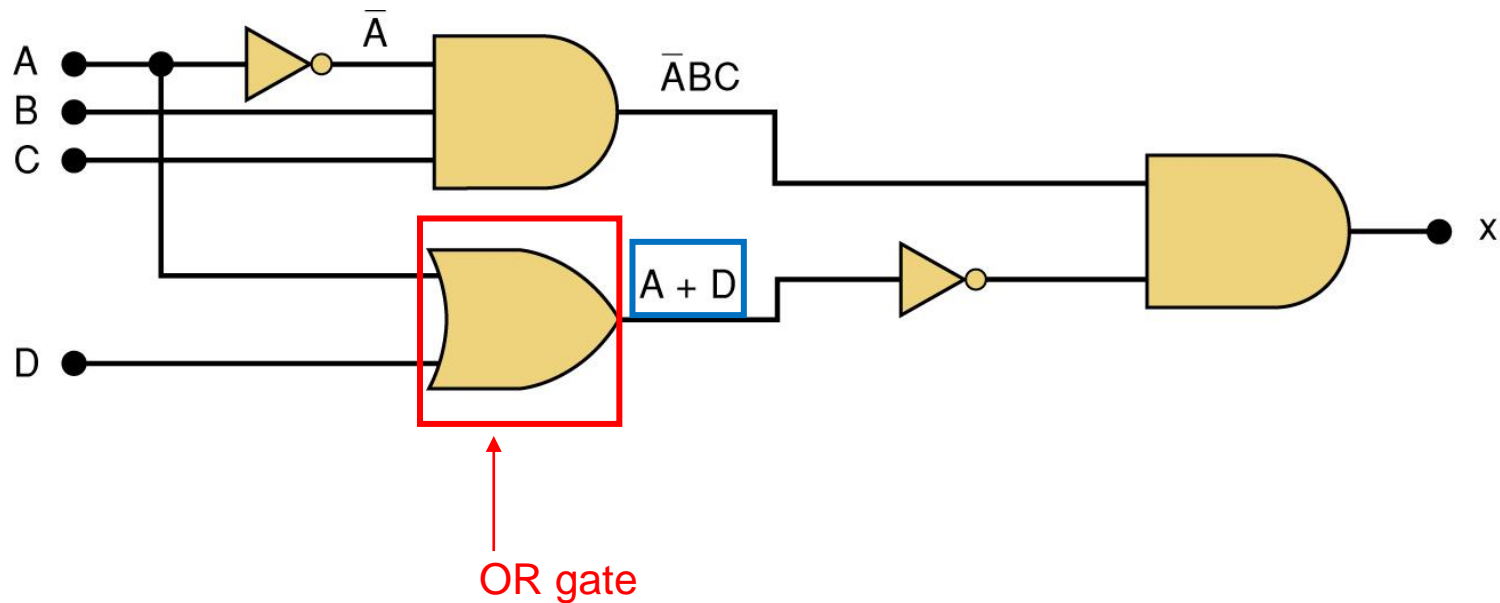


Describing Logic Circuits Algebraically

Example 1

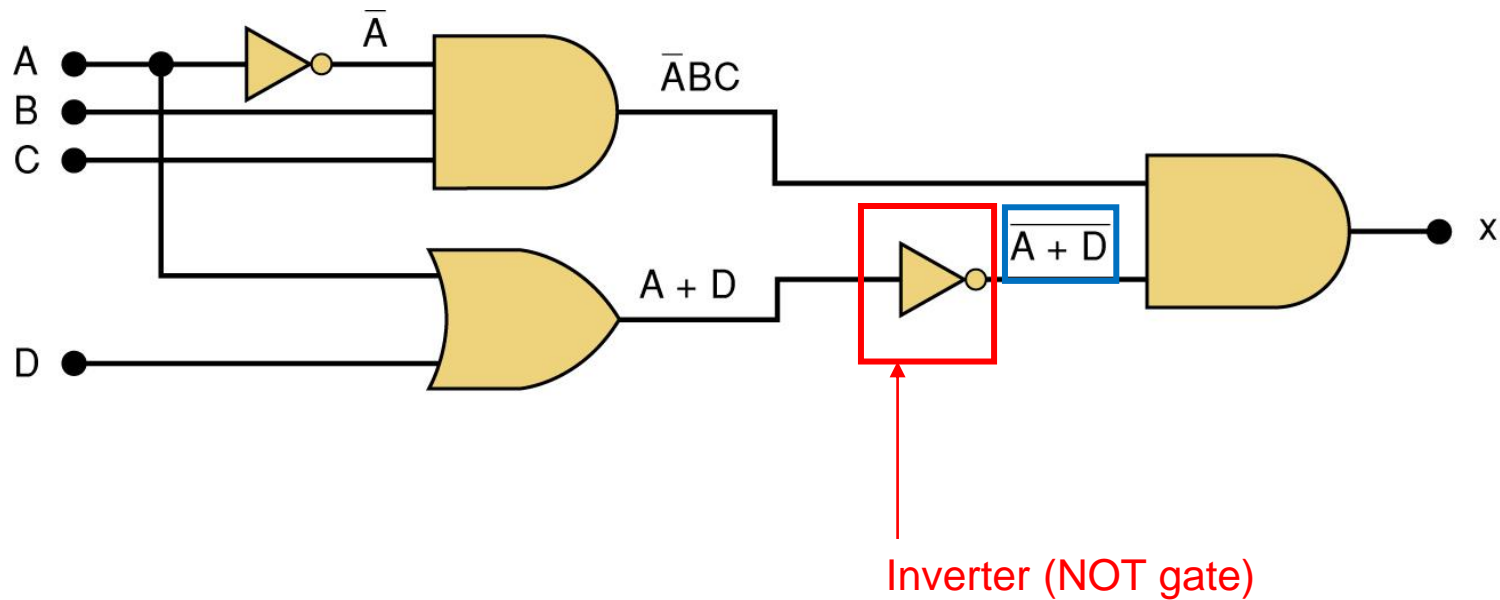


Describing Logic Circuits Algebraically

Example 1

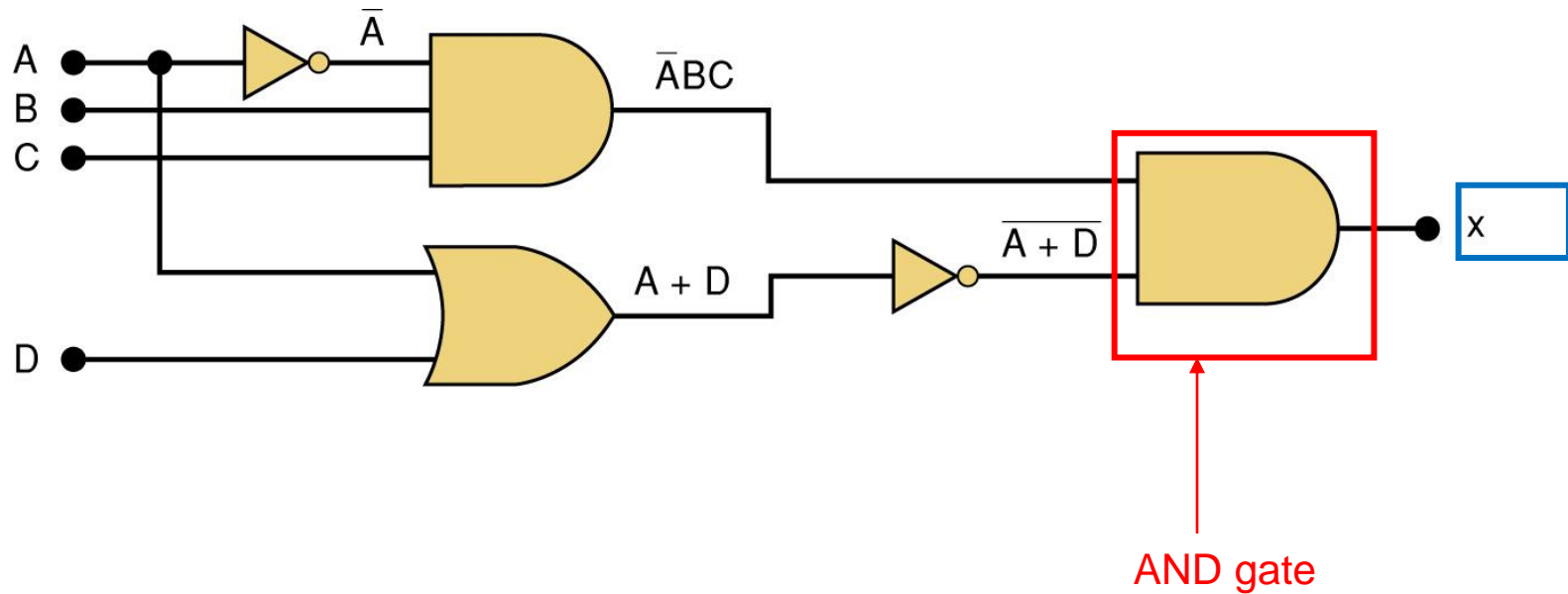


Describing Logic Circuits Algebraically

Example 1

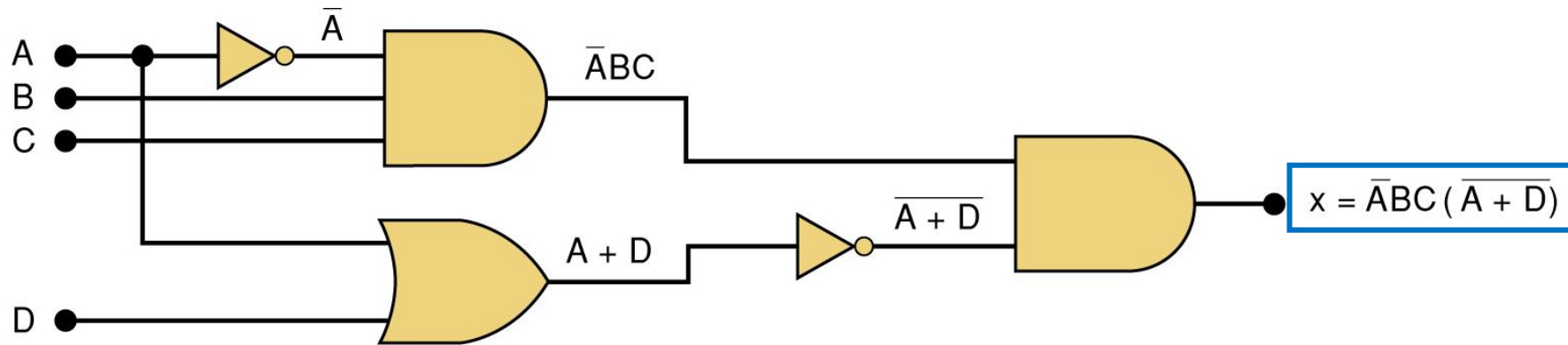

Describing Logic Circuits Algebraically

Exercise

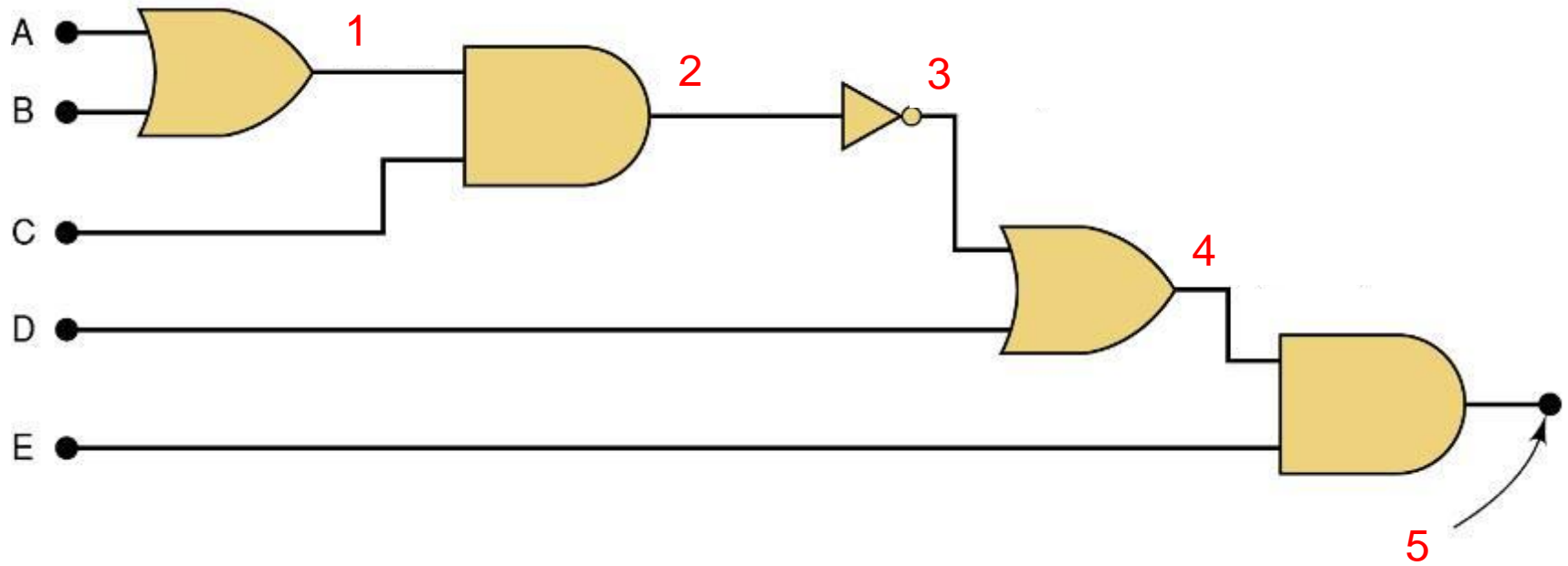

Describing Logic Circuits Algebraically

Exercise - Solution

