

# **XMUT 101**

## **Engineering Technology**

A/Prof. Pawel Dmochowski

School of Engineering and Computer Science  
Victoria University of Wellington

**Victoria**  
UNIVERSITY OF WELLINGTON



*Te Whare Wānanga  
o te Ūpoko o te Ika a Māui*



CAPITAL CITY UNIVERSITY

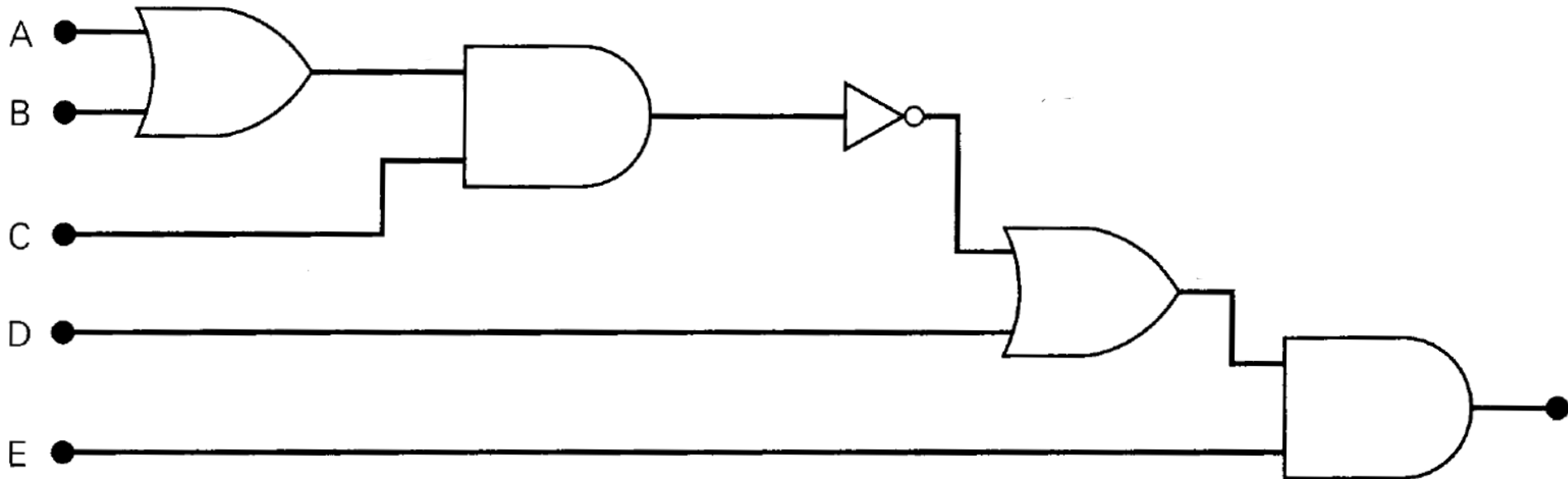
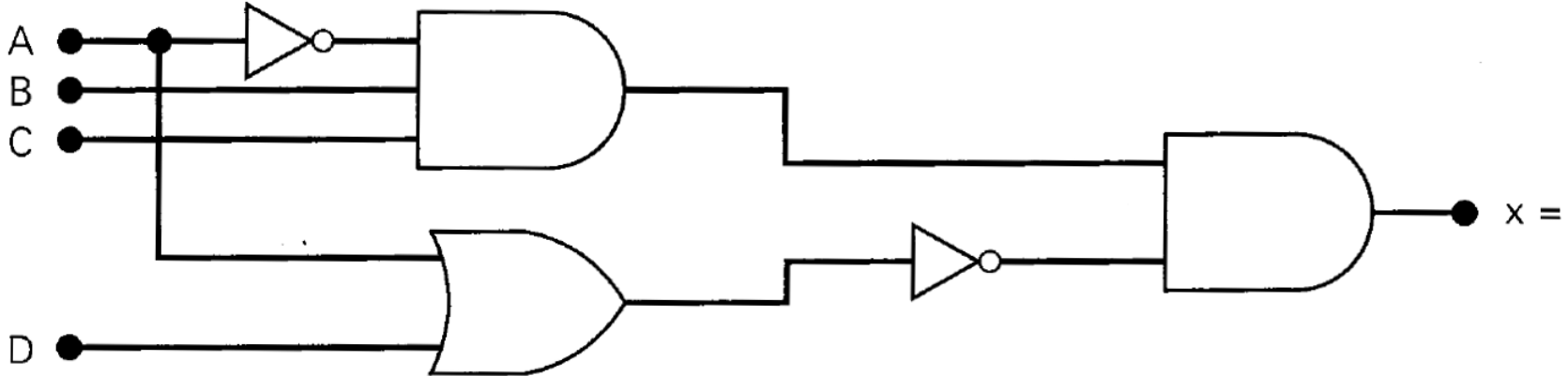
# Review

Write the Boolean expression for the output X


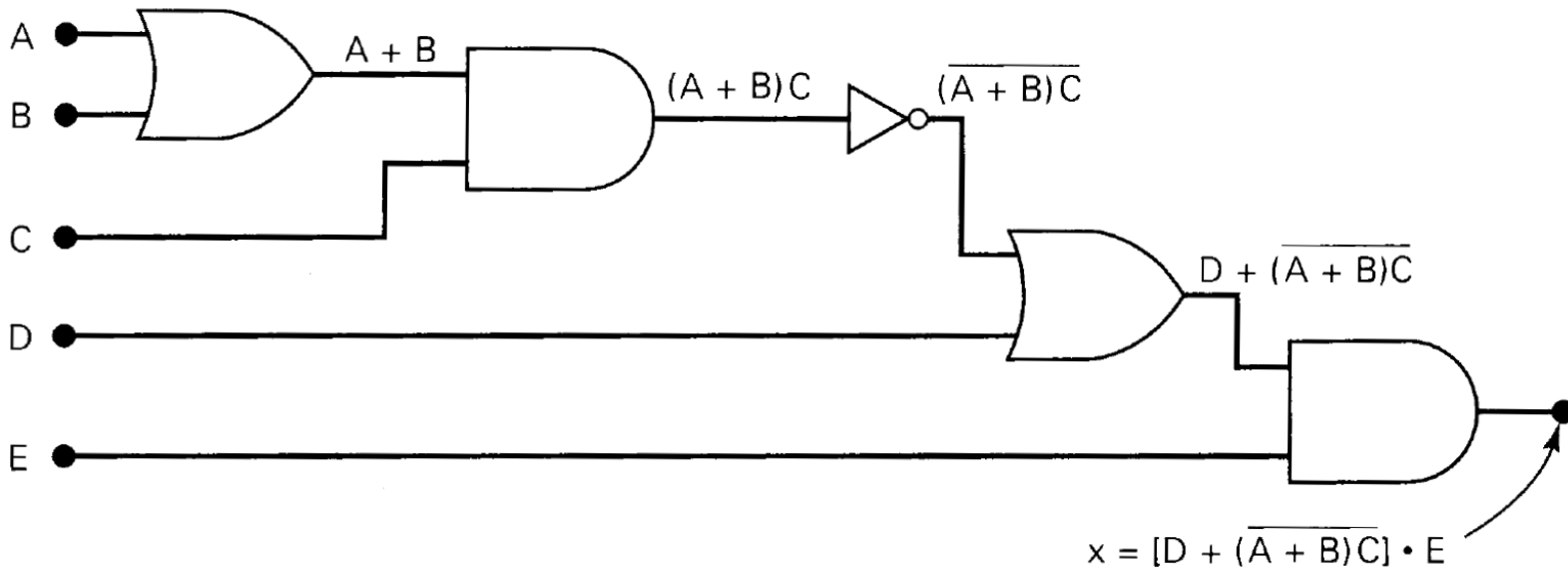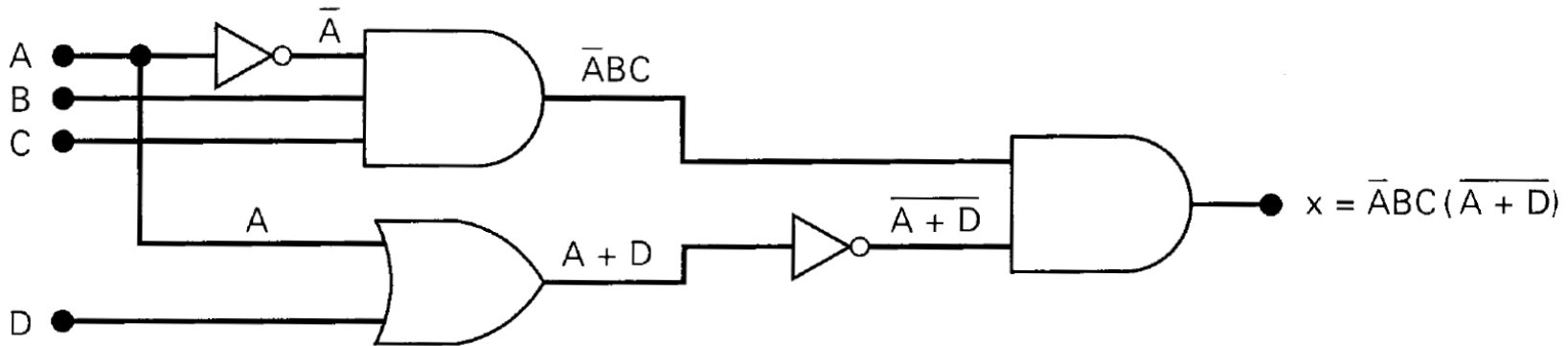
# Review

Evaluate a) for  $A=0, B=1, C=1, D=1$  and b)  $A=0, B=0, C=1, D=1, E=1$



# Review

---


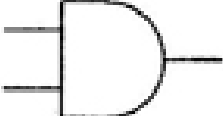
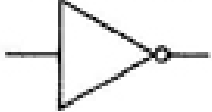
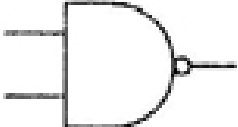



- Draw a circuit diagram to implement  $x=(A+B)(\bar{B}+C)$
- Draw a circuit diagram to implement  $x=AC+B\bar{C}+\bar{A}BC$

# Review

---

- Draw a circuit diagram to implement  $x = \overline{AB(C+D)}$  and determine the output for  $A=B=C=1$  and  $D=0$

# Logic Gates Symbols


Gate	Symbol
OR	
AND	
NOT	
NAND	
NOR	
EX-OR or X-OR	
EX-NOR or X-NOR	

Exclusive OR

Exclusive NOR


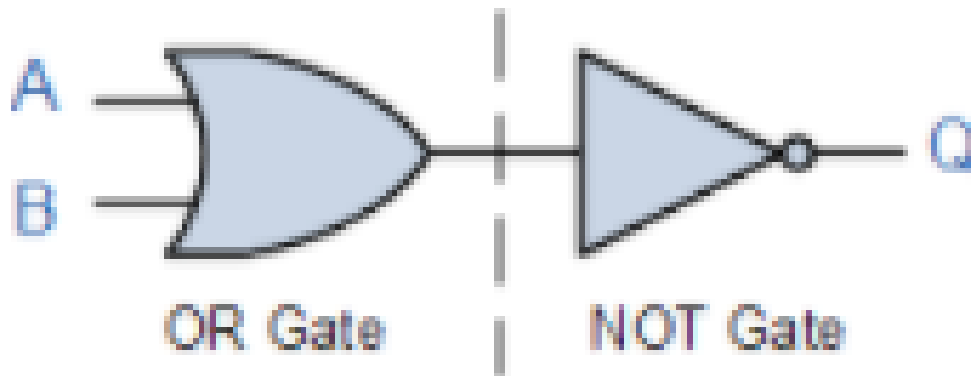
# NOR Gates

- Combine basic OR and NOT gate.
- Not OR - NOR gate is an inverted OR gate.



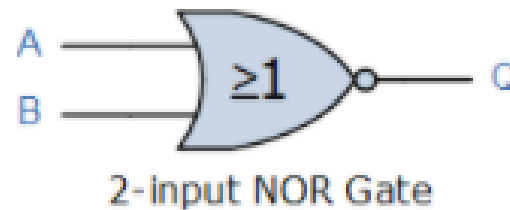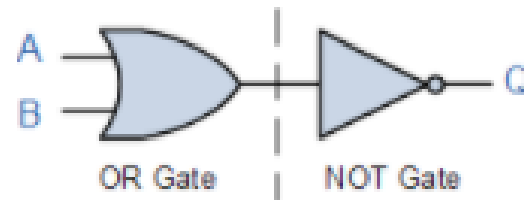
# NOR Gates

- Combine basic OR and NOT gate.
- Not OR - NOR gate is an inverted OR gate.
- An inversion “bubble” is placed at the output of the OR gate.






# (a) NOR symbol

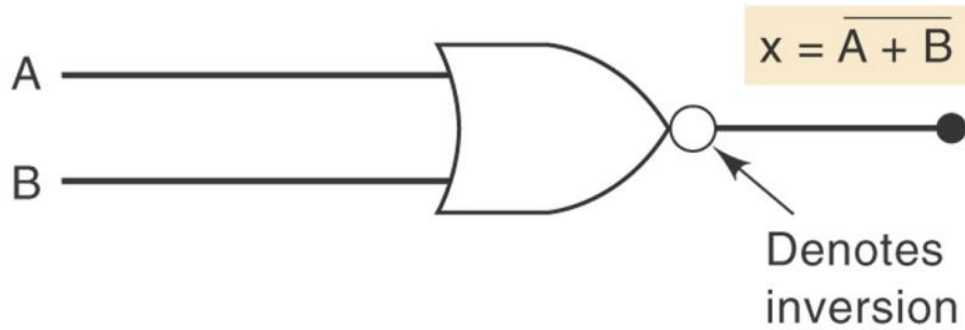
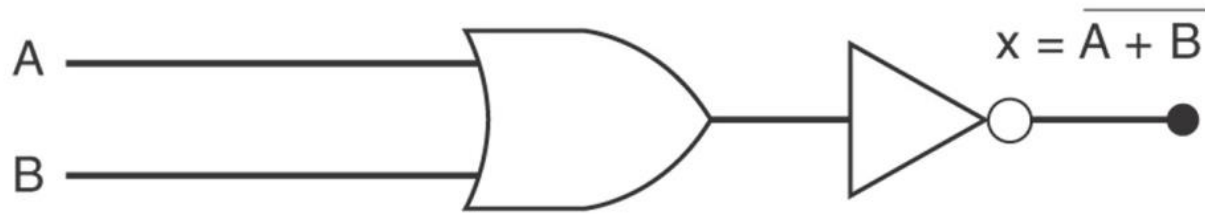
## (b) Equivalent circuit; (c) Truth table.




(b)

		OR		NOR	
A	B	$A + B$		$\overline{A + B}$	
0	0	0		1	
0	1	1		0	
1	0	1		0	
1	1	1		0	

(c)



# NAND Gates

- The NAND gate is an inverted AND gate.


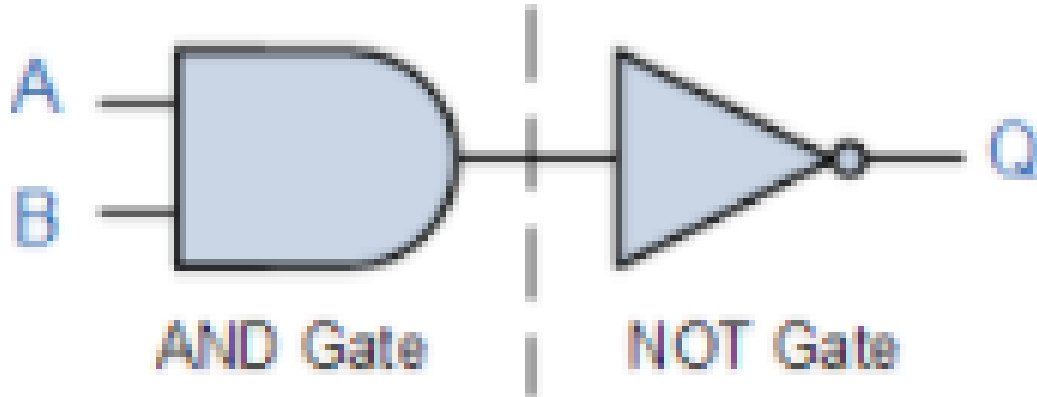

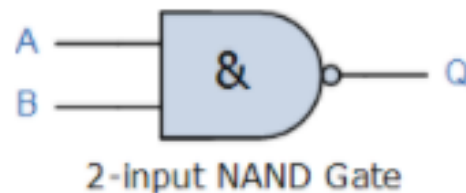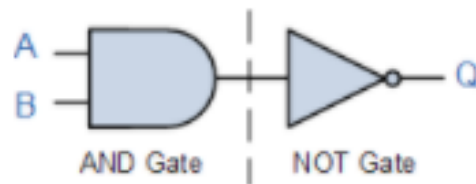
# NAND Gates

- The NAND gate is an inverted AND gate.
- An inversion “bubble” is placed at the output of the AND gate.



# NAND Gates

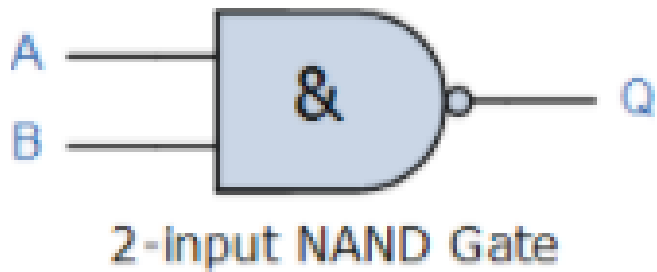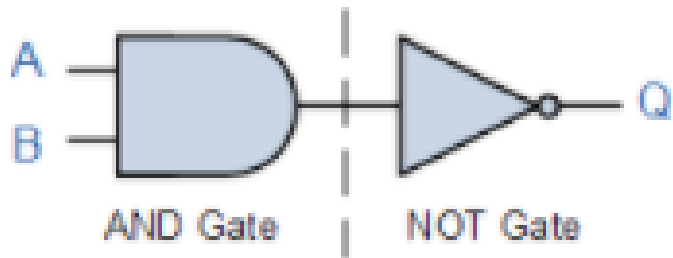

## NAND Truth table

A	B	$A \cdot B$	$\overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


# Review

---

- Draw a circuit diagram to implement  $x = \overline{AB(C+D)}$  using only NOR / NAND gates. Evaluate for  $A=B=C=1$  and  $D=0$
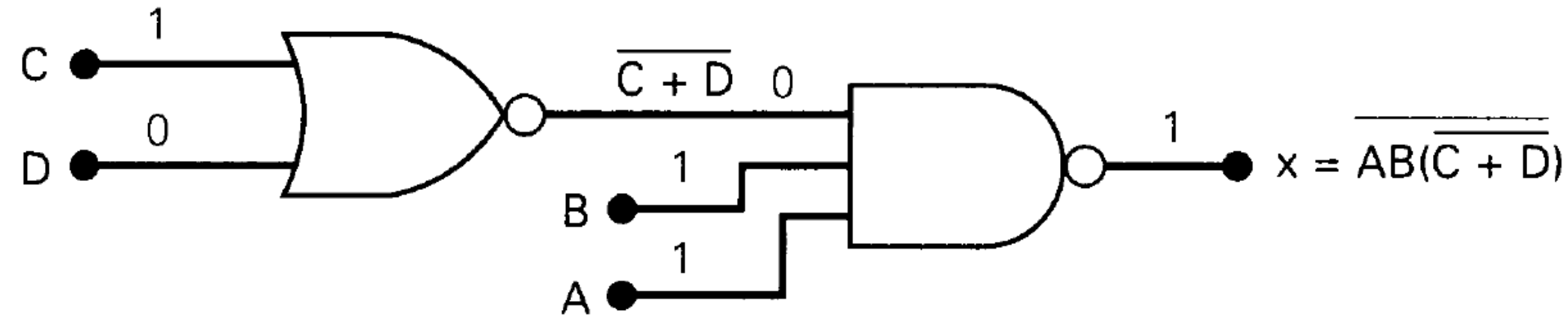
# Review

- Draw a circuit diagram to implement  $x = \overline{AB(C+D)}$  using only NOR / NAND gates. Evaluate for  $A=B=C=1$  and  $D=0$



# Boolean Algebra

- A *Boolean algebra* is defined as a closed algebraic system containing a set  $K$  of two or more elements and the two operators,  $.$  and  $+$ .
- Useful for identifying and *minimizing* circuit functionality
- Identity elements
  - $a + 0 = a$
  - $a . 1 = a$
- $0$  is the identity element for the  $+$  operation.  
 $1$  is the identity element for the  $.$  operation.



# Boolean Algebra for **OR** gate

*OR*

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

# Boolean Algebra for OR, AND

*OR*

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

*AND*

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

# Boolean Algebra for OR, AND & NOT

*OR*

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

*AND*

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

*NOT*

$$\bar{0} = 1$$

$$\bar{1} = 0$$

# Ordering Boolean Functions

---


How to interpret  $A \bullet B + C$ ?

The above expression is read as:

A “AND” B “OR” C
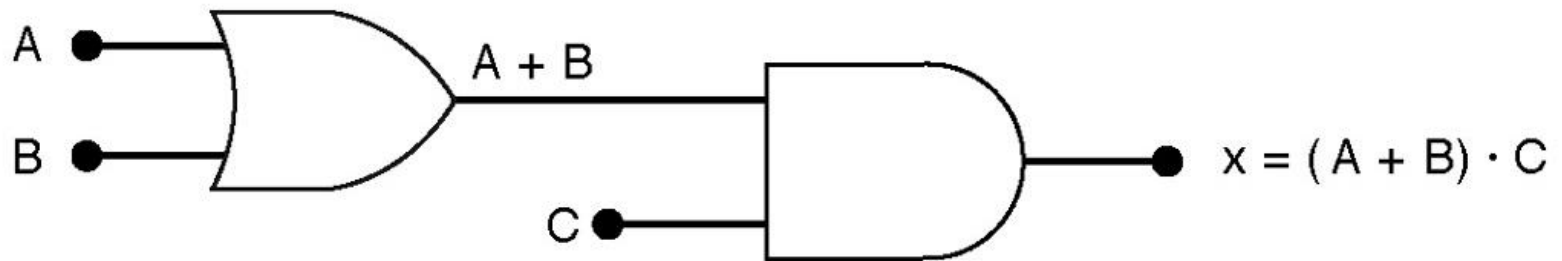
# Ordering Boolean Functions

- How to interpret  $A \bullet B + C$ ?
  - Is it  $A \bullet B$  ORed with  $C$  ?
  - Is it  $A$  ANDed with  $B + C$  ?
- Order of precedence for Boolean algebra:  
AND before OR.
- Note that **parentheses** are needed here :



# Commutativity and Associativity

- The **Commutative** Property:

For every a and b,

$$(1) a + b = b + a$$

$$(2) a \cdot b = b \cdot a$$

- The **Associative** Property:

For every a, b, and c,

$$(1) a + (b + c) = (a + b) + c$$

$$(2) a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

# Distributivity of the Operators and Complements

- The **Distributive** Property:

For every  $a$ ,  $b$ , and  $c$  in  $K$ ,

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

- The **Existence** of the Complement:

For every  $a$  in  $K$  there exists a unique element called  $\bar{a}$

(*complement of  $a$* ) such that,

$$a + \bar{a} = 1$$

$$a \cdot \bar{a} = 0$$

# Distributivity of the Operators and Complements

- The Distributive Property:

For every  $a$ ,  $b$ , and  $c$  in  $K$ ,

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

- The Existence of the Complement:

For every  $a$  in  $K$  there exists a unique element called  $a'$  (*complement of  $a$* ) such that,

$$a + \bar{a} = 1$$

$$a \cdot \bar{a} = 0$$

- To simplify notation, the  $\cdot$  operator is frequently omitted. When two elements are written next to each other, the AND ( $\cdot$ ) operator is implied...

$$a + b \cdot c = (a + b) \cdot (a + c)$$


$$a + bc = (a + b)(a + c)$$



# Duality

- The principle of *duality* is often a helpful concept – it is symmetry present properties and theorems.
- In Boolean algebra we form a dual expression
  - swap + for . operators, and vice versa
  - swap 1s for 0s and vice versa
- Example: the dual of  $a(b + c) = ab + ac$   
is  $a + (bc) = (a + b)(a + c)$
- We say that duality holds if both are true.  
(as we will soon see, both are true, so indeed, duality holds for this expression)

# Involution

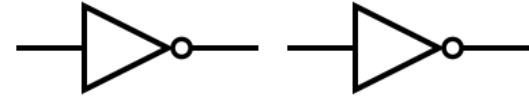

- This theorem states:  
 $\overline{\overline{a}} = a$
- Remember that  $a\overline{a} = 0$  and  $a + \overline{a} = 1$ .
  - Therefore,  $\overline{a}$  is the complement of  $a$  and  $a$  is also the complement of  $\overline{a}$ .
  - As the complement of  $\overline{a}$  is unique, it follows that  $\overline{\overline{a}} = a$ .
- Taking the double inverse of a value will give the initial value.

# Absorption

---

- This theorem states:

$$a + ab = a$$

$$a(a+b) = a$$

# Absorption

---

- This theorem states:

$$a + ab = a$$

$$a(a+b) = a$$

- To prove the first half of this theorem:

$$a + ab = a \cdot 1 + ab$$

$$= a (1 + b)$$

$$= a (b + 1)$$

$$= a (1)$$

$$a + ab = a$$

# DeMorgan's Theorem

---

- A key theorem in simplifying Boolean algebra expression is DeMorgan's Theorem. It states:

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(ab)} = \bar{a} + \bar{b}$$

# DeMorgan's Theorem

- A key theorem in simplifying Boolean algebra expression is DeMorgan's Theorem. It states:

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(ab)} = \bar{a} + \bar{b}$$

- Complement the expression  $(a(b + z(x + \bar{a})))$  and simplify.

$$\begin{aligned}\overline{(a(b+z(x + \bar{a})))} &= \bar{a} + \overline{(b + z(x + \bar{a}))} \\ &= \bar{a} + \bar{b}(z(x + \bar{a})) \\ &= \bar{a} + \bar{b}(\bar{z} + \overline{(x + a)}) \\ &= \bar{a} + \bar{b}(\bar{z} + \bar{x}\bar{a}) \\ &= \bar{a} + \bar{b}(\bar{z} + \bar{x}a)\end{aligned}$$

# DeMorgan's Theorem – Exercise

---

Simplify the expression:

$$\overline{\overline{(x \bar{y})} (\bar{y} + z)}$$

# DeMorgan's Theorem – Exercise

Solution:

$$\overline{\overline{(X \cdot \bar{Y})} (\bar{Y} + Z)}$$

$$\overline{(\overline{X \cdot \bar{Y}}) \cdot (\overline{\bar{Y} + Z})}$$

$$\overline{(\overline{X \cdot \bar{Y}}) + (\overline{\bar{Y} + Z})}$$

$$(X \cdot \bar{Y}) + (\bar{Y} \cdot \bar{Z})$$

$$(X \cdot \bar{Y}) + (Y \cdot \bar{Z})$$

$$= X\bar{Y} + Y\bar{Z}$$



# DeMorgan: exercises

---

$$z = \overline{A + \overline{B} \cdot C}$$

$$\omega = \overline{(A + BC) \cdot (D + EF)}$$

# DeMorgan: exercises

$$z = \overline{A + \overline{B} \cdot C}$$

$$= \overline{A} \cdot \overline{(\overline{B} \cdot C)}$$

$$= \overline{A} \cdot (\overline{\overline{B}} + \overline{C})$$

$$= \overline{A} \cdot (B + \overline{C})$$

$$\omega = \overline{(A + BC) \cdot (D + EF)}$$

$$= \overline{(A + BC)} + \overline{(D + EF)}$$

$$= (\overline{A} \cdot \overline{BC}) + (\overline{D} \cdot \overline{EF})$$

$$= [\overline{A} \cdot (\overline{B} + \overline{C})] + [\overline{D} \cdot (\overline{E} + \overline{F})]$$

$$= \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{D}\overline{E} + \overline{D}\overline{F}$$

# Boolean Algebra Laws

	Name of Law	Properties
1.	Identity Law	$A+0=A$ ; $A+1=1$ ; $A.0=0$ ; $A.1=A$
2.	Commutative Law	$A.B = B.A$ ; $A+B = B+A$
3.	Associative Law	$A.(B.C) = A.B.C$ ; $A+(B+C) = A+B+C$
4.	Idempotent Law	$A.A = A$ ; $A+A = A$
5.	Double Negative Law	$A'' = A$
6.	Complement Law	$A.A' = 0$ ; $A+A' = 1$
7.	Law of Union	$A+1 = 1$ ; $A+0 = A$
8.	De Morgan's Theorem	$(AB)' = A'+B'$ ; $(A+B)' = A'.B'$
9.	Distributive Law	$A.(B+C) = (A.B) + (A.C)$ ; $A+(BC) = (A+B).(A+C)$
10.	Absorption Law	$A.(A+B) = A$ ; $A+(A.B) = A$
11.	Common Identities Law	$A.(A'+B) = AB$ ; $A+(A'B) = A+B$

**Example 1:** Simplify the given Boolean expression.

---

$$C + (BC)'$$

**Example 1:** Simplify the given Boolean expression.

---

$$C + (BC)' \rightarrow \overline{BC}$$

# Example 1

Simplify the expression:  $C + (BC)'$   $\rightarrow$   $\overline{BC}$

Solution:

$C + (BC)'$

Rules Used

Apply DeMorgan's Theorem to the  $(BC)'$  term

9. DeMorgan's Theorem

$(AB)' = A'+B'$ ;  $(A+B)' = A'.B'$

# Example 1

Simplify the expression:  $C + (BC)'$   $\rightarrow$   $\overline{BC}$

Solution:

$C + (BC)'$

Rules Used

Step 1:  $C + (B' + C')$

9) DeMorgan's Law

9. DeMorgan's Theorem

$(AB)' = A' + B'$ ;  $(A + B)' = A' \cdot B'$

# Example 1

Simplify the expression:  $C + (BC)'$   $\rightarrow$   $\overline{BC}$

Solution:

$$C + (BC)'$$

Step 1:  $C + (B' + C')$

Step 2:  $C + (C' + B')$

Rules Used

8) DeMorgan's Law

2) Commutative Law

2.	Commutative Law	$A.B = B.A;$ $A+B = B+A$



# Example 1

Simplify the expression:  $C + (BC)'$   $\longrightarrow$   $\overline{BC}$

Solution:

$$C + (BC)'$$

**Step 1:**  $C + (B' + C')$

**Step 2:**  $C + (C' + B')$

**Step 3:**  $C + C' + B'$

Rules Used

8) De Morgan's Law

2) Commutative

3) Associative Laws

3.	Associative Law	$A.(B.C) = A.B.C$ ; $A+(B+C) = A+B+C$

# Example 1

Simplify the expression:  $C + (BC)'$   $\rightarrow$   $\overline{BC}$

Solution:

$$C + (BC)'$$

Step 1:  $C + (B' + C')$

Step 2:  $C + (C' + B')$

Step 3:  $C + C' + B'$

Step 4:  $1 + B'$

Rules Used

8) DeMorgan's Law

2) Commutative

3) Associative Laws

6) Complement Law

6. Complementary Law

$A.A' = 0$ ;  $A+A' = 1$

# Example 1

Simplify the expression:  $C + (BC)'$   $\rightarrow$   $\overline{BC}$

Solution:

$$C + (BC)'$$

Step 1:  $C + (B' + C')$

Step 2:  $C + (C' + B')$

Step 3:  $C + C' + B'$

Step 4:  $1 + B'$

Step 5:  $= 1$

Rules Used

8) DeMorgan's Law

2) Commutative

3) Associative Laws

6) Complement Law

1) Identity Law

1. Identity Law

$A+0=A$ ;  $A+1=1$ ;  $A.0=0$ ;  $A.1=A$

**Example 2:** Simplify the given Boolean expression.

---

$$(AB)'(A'+B)(B'+B)$$

## Example 2: Simplify the given Boolean expression.

$$(AB)'(A'+B)(B'+B)$$

	Name of Law	Properties
1.	Identity Law	$A+0=A$ ; $A+1=1$ ; $A.0=0$ ; $A.1=A$
2.	Commutative Law	$A.B = B.A$ ; $A+B = B+A$
3.	Associative Law	$A.(B.C) = A.B.C$ ; $A+(B+C) = A+B+C$
4.	Idempotent Law	$A.A = A$ ; $A+A = A$
5.	Double Negative Law	$A'' = A$
6.	Complement Law	$A.A' = 0$ ; $A+A' = 1$
7.	Law of Union	$A+1 = 1$ ; $A+0 = A$
8.	DeMorgan's Theorem	$(AB)' = A'+B'$ ; $(A+B)' = A'.B'$
9.	Distributive Law	$A.(B+C) = (A.B) + (A.C)$ ; $A+(BC) = (A+B).(A+C)$
10.	Absorption Law	$A.(A+B) = A$ ; $A+(A.B) = A$
11.	Common Identities Law	$A.(A'+B) = AB$ ; $A+(A'.B) = A+B$

## Example 2: Simplify the given Boolean expression.

$$(AB)'(A'+B)(B'+B)$$

Solution:

$$(AB)'(A'+B)(B'+B)$$

Rules Used

Step 1:  $(AB)'(A'+B)(1)$

6) Complement Law

6. Complement Law

$$A.A' = 0; A+A' = 1$$

## Example 2: Simplify the given Boolean expression.

$$(AB)'(A'+B)(B'+B)$$

Solution:

$$(AB)'(A'+B)(B'+B)$$

Rules Used

Step 1:  $(AB)'(A'+B)(1)$

6) Complementary Law

Step 2:  $(AB)'(A'+B)$

1) Identity Law

1. Identity Law

$A+0=A$ ;  $A+1=1$ ;  $A.0=0$ ;  $A.1=A$

## Example 2: Simplify the given Boolean expression.

$$(AB)'(A'+B)(B'+B)$$

### Solution:

$$(AB)'(A'+B)(B'+B)$$

### Rules Used

Step 1:  $(AB)'(A'+B)(1)$

6) Complementary Law

Step 2:  $(AB)'(A'+B)$

1) Identity Law

Step 3:  $(A'+B')(A'+B)$

8) DeMorgan's Theorem

8. DeMorgan's Theorem

$$(AB)' = A'+B'; \quad (A+B)' = A'.B'$$



## Example 2: Simplify the given Boolean expression.

$$(AB)'(A'+B)(B'+B)$$

### Solution:

$$(AB)'(A'+B)(B'+B)$$

Step 1:  $(AB)'(A'+B)(1)$

Step 2:  $(AB)'(A'+B)$

Step 3:  $(A'+B')(A'+B)$

Step 4:  $A' + B'B$

### Rules Used

6) Complementary Law

1) Identity Law

8) DeMorgan's Theorem

9) Distributive Law

9. Distributive Law

$$A.(B+C) = (A.B) + (A.C);$$
$$A+(BC) = (A+B).(A+C)$$

## Example 2: Simplify the given Boolean expression.

$$(AB)'(A'+B)(B'+B)$$

### Solution:

$$(AB)'(A'+B)(B'+B)$$

### Rules Used

Step 1:  $(AB)'(A'+B)(1)$

6) Complementary Law

Step 2:  $(AB)'(A'+B)$

1) Identity Law

Step 3:  $(A'+B')(A'+B)$

8) DeMorgan's Theorem

Step 4:  $A' + B'B$

9) Distributive Law

Step 5:  $= A'$

6) Complement Law

6. Complement Law

$$A.A' = 0; A+A' = 1$$

# Exercise

Use the Boolean rules to simplify the following expressions:

$$(a) \quad X = ABC + \overline{A}B + AB\overline{C}$$

$$(b) \quad X = \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$$

$$(c) \quad AB + \overline{A}C + BC = AB + \overline{A}C$$

$$(d) \quad (A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$$

## Exercise 6.2

---

Use the Boolean rules to simplify the following expressions:

$$(i) \quad AB + AC + ABC \qquad (ii) \quad AB + A(\overline{B} + C) + AB\overline{C}$$

$$(iii) \quad \overline{A}BC + A\overline{B}C + ABC + AB\overline{C} + \overline{A}\overline{B}\overline{C}$$

$$(iv) \quad \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}B C$$

Simplify and draw the circuit diagram for


---

$$x = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

Simplify and draw the circuit diagram for

$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Trick: copy terms (remember:  $X+X=X$ )

$$\begin{aligned} x &= \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \\ &= \bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC \end{aligned}$$


Simplify and draw the circuit diagram for

$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Trick: 'duplicate' terms (remember:  $X+X=X$ )

$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= \boxed{\bar{A}BC + ABC} + \boxed{A\bar{B}C + ABC} + \boxed{AB\bar{C} + ABC}$$

$$= \boxed{BC(\bar{A} + A)} + \boxed{AC(\bar{B} + B)} + \boxed{AB(\bar{C} + C)}$$

Simplify and draw the circuit diagram for

$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$


Trick: copy terms (remember:  $X+X=X$ )

$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= \bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC$$

$$= BC(\bar{A} + A) + AC(\bar{B} + B) + AB(\bar{C} + C)$$


$$= BC + AC + AB$$

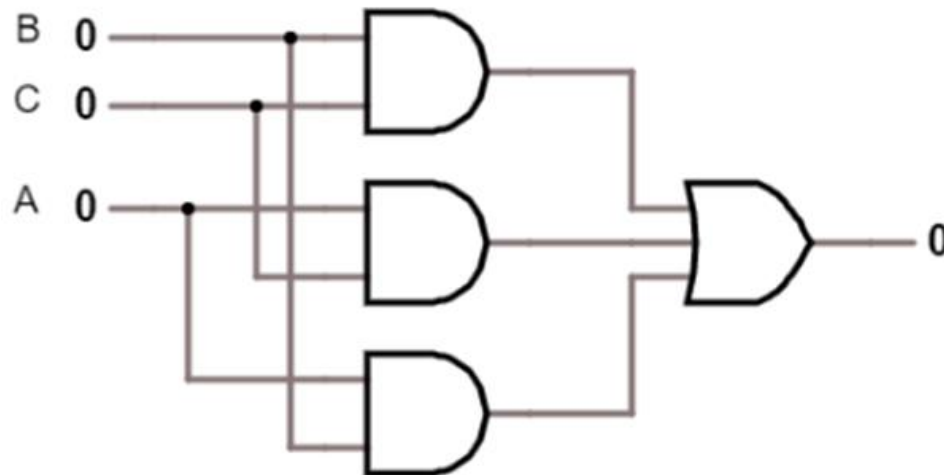



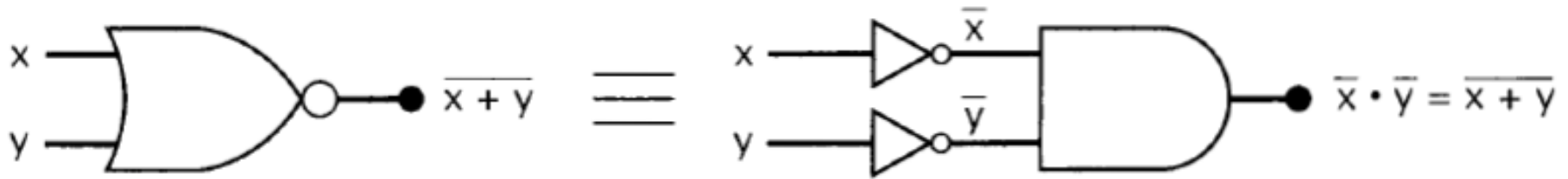
# DeMorgan's Theorem and NOR gates

- What does DeMorgan's theorem imply about NOR gates?




- Another symbol for the NOR function

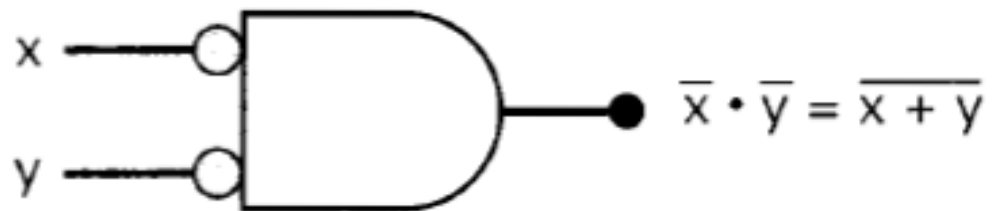

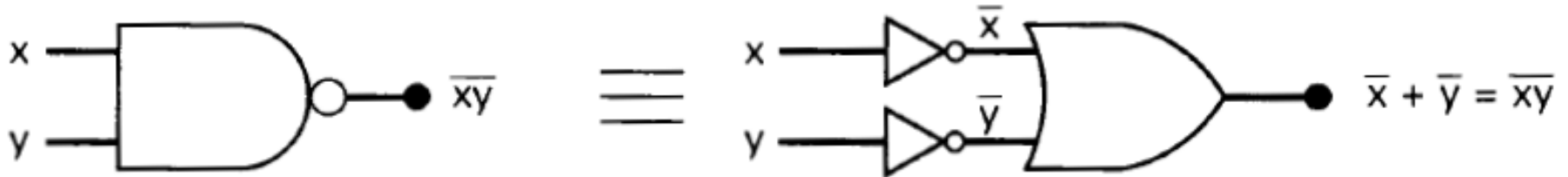
# DeMorgan's Theorem and NAND gates

- What does DeMorgan's theorem imply about NAND gates?




- Another symbol for the NAND function

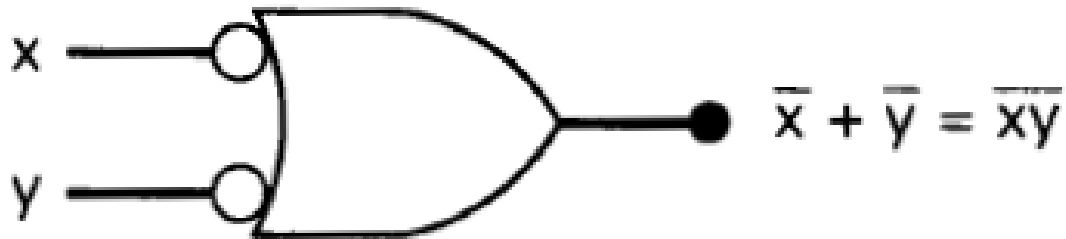



## Exclusive OR and Exclusive NOR Circuits

- The exclusive OR, abbreviated XOR produces a HIGH output whenever the two inputs are at opposite levels.
- The exclusive NOR, abbreviated XNOR produces a HIGH output whenever the two inputs are at the same level.
- XOR and XNOR outputs are opposite.


**FIGURE 4-20** (a) Exclusive-OR circuit and truth table; (b) traditional XOR gate symbol; (c) IEEE/ANSI symbol for XOR gate.

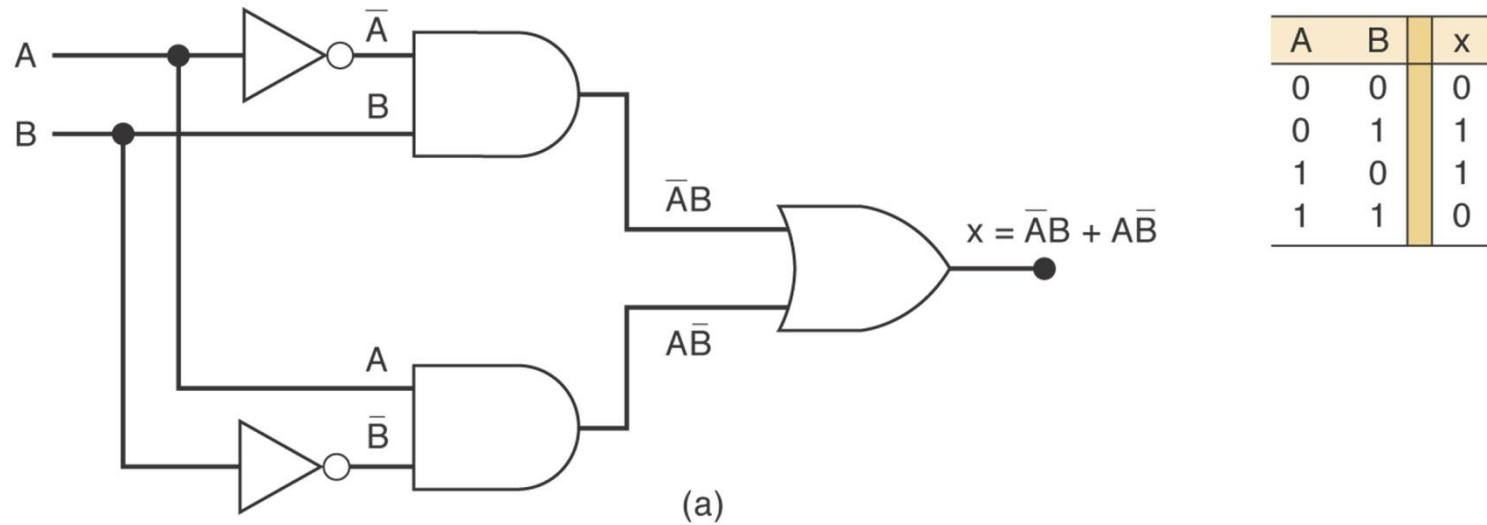



XOR gate symbols

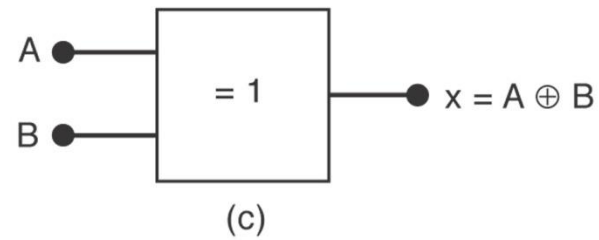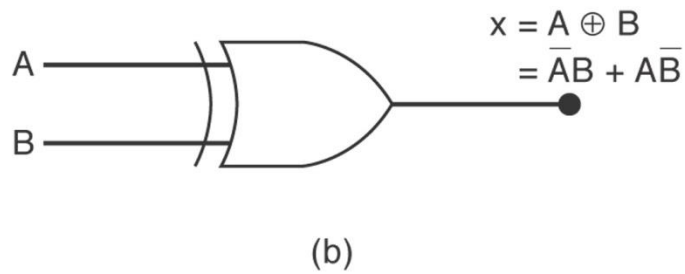



**FIGURE 4-21** (a) Exclusive-NOR circuit; (b) traditional symbol for XNOR gate; (c) IEEE/ANSI symbol.

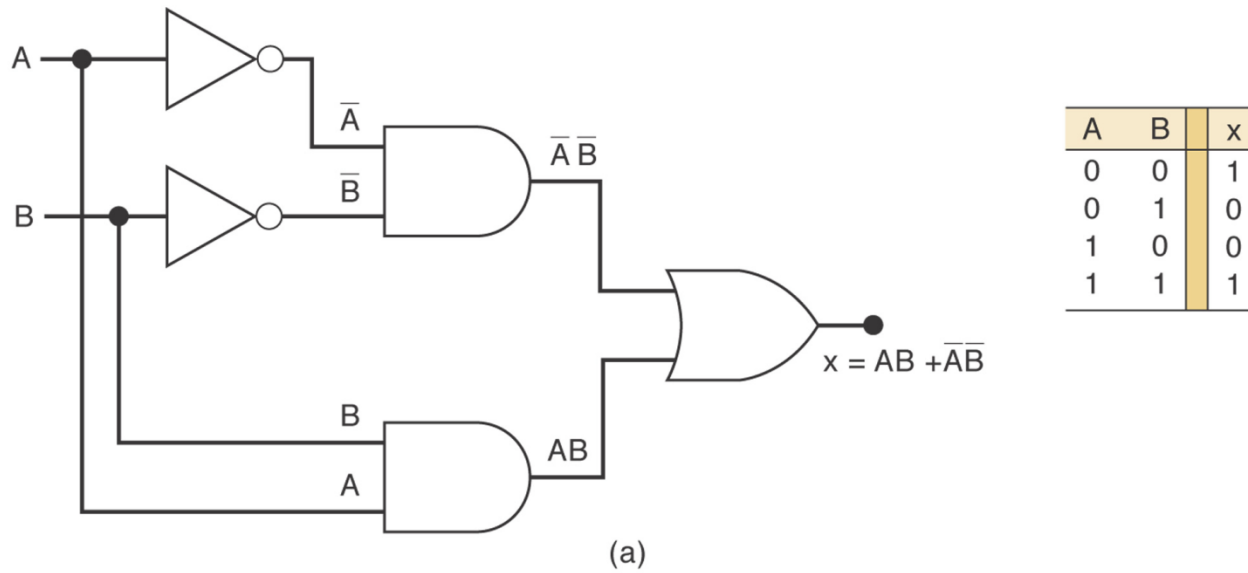

XNOR gate symbols

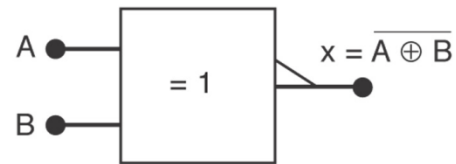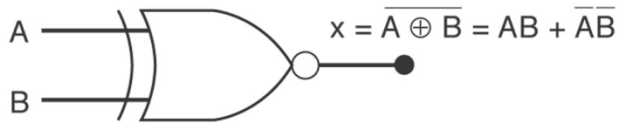

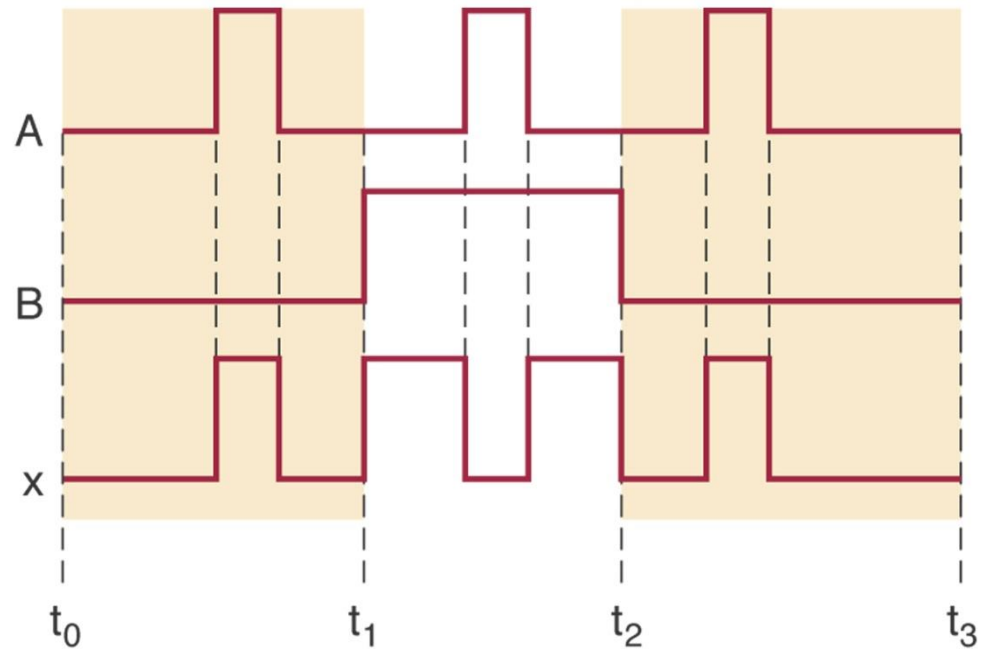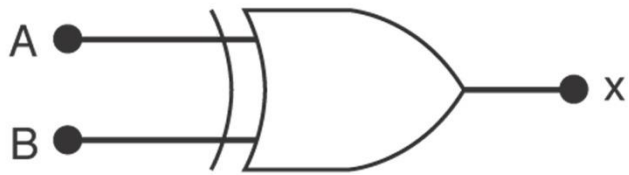
# Determine the O/P waveform of the circuit below:



O/P Hi when I/P at different levels

**Design a circuit so that the O/P will only be HI when the combination of two sets of two bit binary numbers are equal.**

$x_1$	$x_0$	$y_1$	$y_0$	$z$ (Output)
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

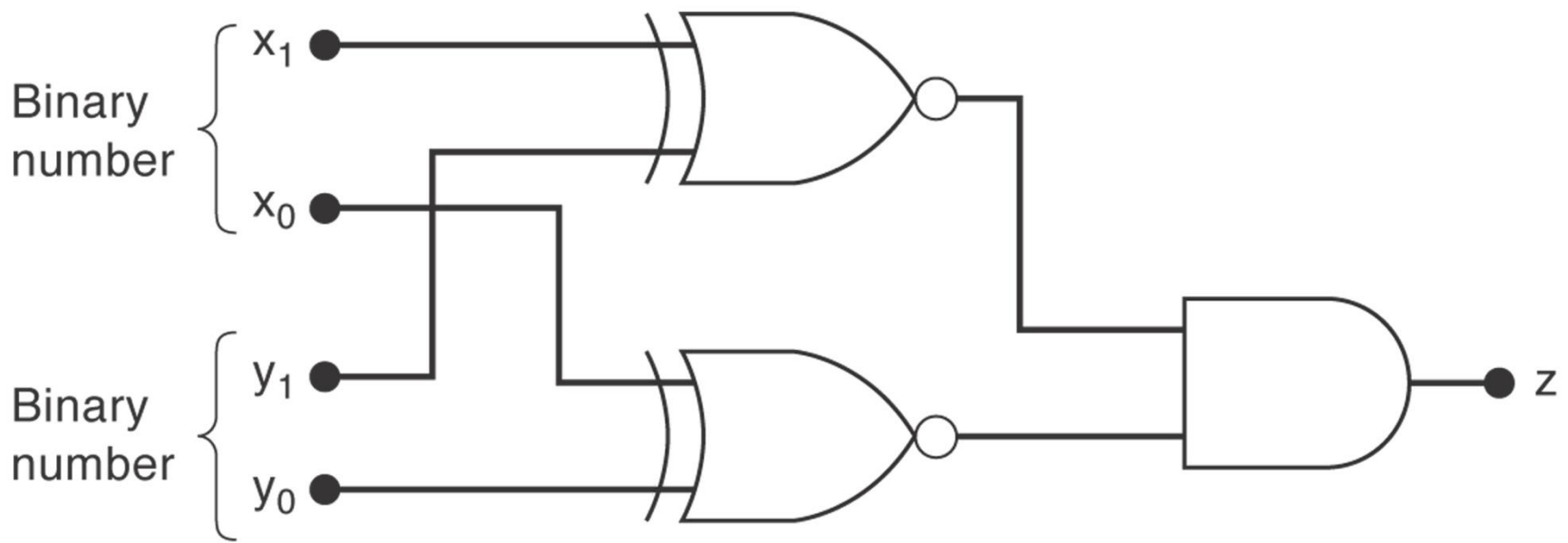



# Parity

---

- XOR and XNOR gates are often used in parity generators and parity checkers
- (more on this in future courses!)