

ECEN202

2024

**Analogue to digital and Digital to Analog
Conversion.**

Lecture 1

A-D/D-A


- Conversion between analogue and digital signals is common. The following aspects will be examined:
 - DAC and ADC
 - Different conversion methods
 - Sampling
 - Analogue multiplexing
 - Analogue interfacing

Interfacing With the Analog World

- A review of the difference between digital and analog quantities
 - Digital quantities - values can take on one of several discrete values. Discrete
 - Analog quantities - values can take on an infinite number of values. Continuous.

Interfacing With the Analog World

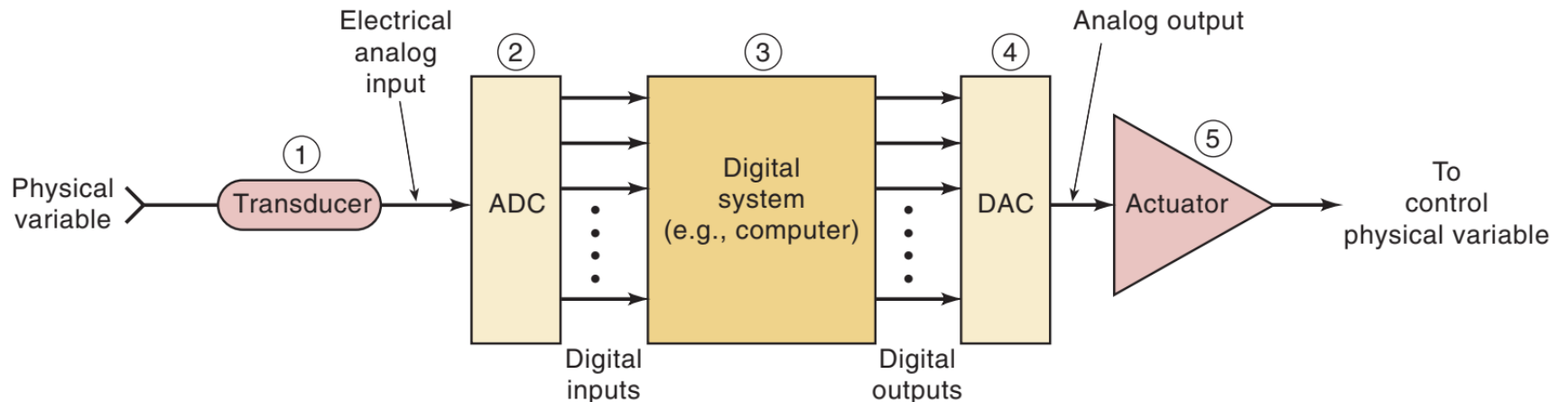
- Transducer
- ADC
- Computer
- DAC
- Actuator



Digital to Analog Conversion

- The conversion process:
 - Digital code is converted to a voltage or current proportional to the digital code
 - Voltage reference used to determine the full scale O/P.
 - Analog O/P = $K \times$ digital I/P
where K is the proportionality factor
 - "Pseudo analog" as O/P cannot take on continuous values
 - Bipolar DAC's: Use 2's compliment to represent negative voltages

Four-bit DAC with voltage output.

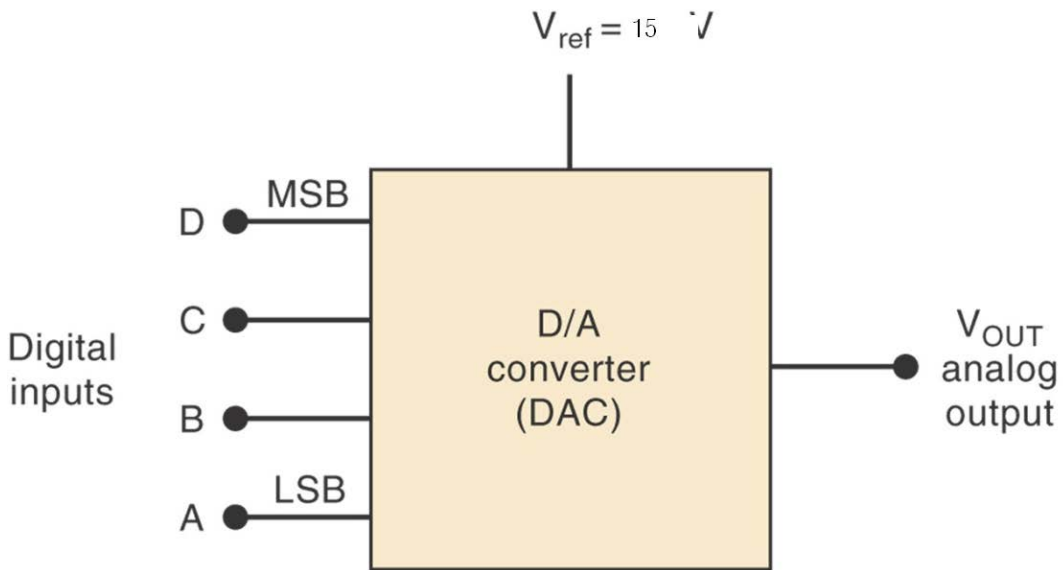

D	C	B	A	V_{OUT}		
0	0	0	0	0	Volts	
0	0	0	1	1	↓ Volts	
0	0	1	0	2		
0	0	1	1	3		
0	1	0	0	4		
0	1	0	1	5		
0	1	1	0	6		
0	1	1	1	7		
<hr/>						
1	0	0	0	8		
1	0	0	1	9		
1	0	1	0	10		
1	0	1	1	11		
1	1	0	0	12		
1	1	0	1	13		
1	1	1	0	14		
1	1	1	1	15	Volts	

(b)

Problem 1: A 5-bit DAC has a current O/P. For a digital I/P of 10100 an O/P current of 10 mA is produced. What is:

(i) I_{out} for a digital I/P of 11101 ?

(ii) The full scale O/P ?

Problem 1: A 5-bit DAC has a current O/P. For a digital I/P of 10100 an O/P current of 10 mA is produced. What is:

(i) I_{out} for a digital I/P of 11101 ?

(ii) The full scale O/P ?

Answer:

(i) 10100_2 is decimal 20_{10} .

Thus $K = 10\text{mA}/20 = 0.5\text{mA}$

So for $11101_2 = 29_{10}$ we have $O/P = 29 \times 0.5\text{mA} = 14.5 \text{ mA}$

(ii) Thus full scale O/P: $11111 = 31_{10}$


Thus $O/P = 31 \times 0.5 \text{ mA} = 15.5 \text{ mA}$.

Resolution (Step size)

The smallest change that can happen in the analog output as a result of change in the digital input.

The resolution is always equal to the weight of the LSB and is also referred to as the step size because it is the amount that V_{OUT} will change as the digital input value is changed from one step to the next.

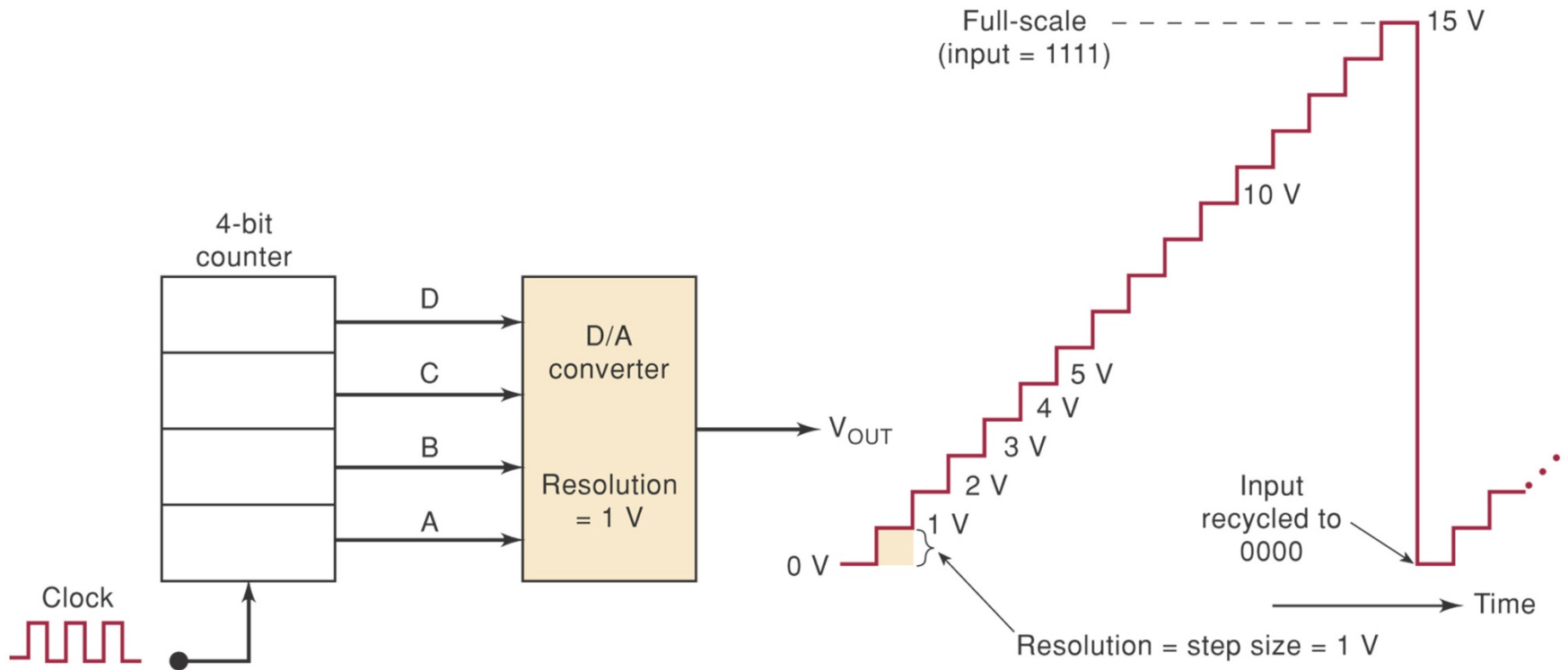Output waveforms of a DAC as inputs are provided by a binary counter



Resolution

Difference in O/P voltage caused by a single code bit change on the I/P.

$$\begin{aligned} \text{Resolution} &= \frac{\text{Full scale analog output}}{2^n - 1} \\ &= K \end{aligned}$$

Percentage Resolution

Often useful to express resolution as a % of the full scale output:

$$\% \text{ Resolution} = \text{Step Size} / \text{Full Scale} \times 100\%$$

$$\text{E.g.: } 1\text{V step} / 15\text{ V Full scale} \times 100\% = 6.67\%$$

Questions ?


A. How do we construct a digital to analog converter ?

B. How do we use them in practice ?


C. What are they useful for ?

What are they useful for ?

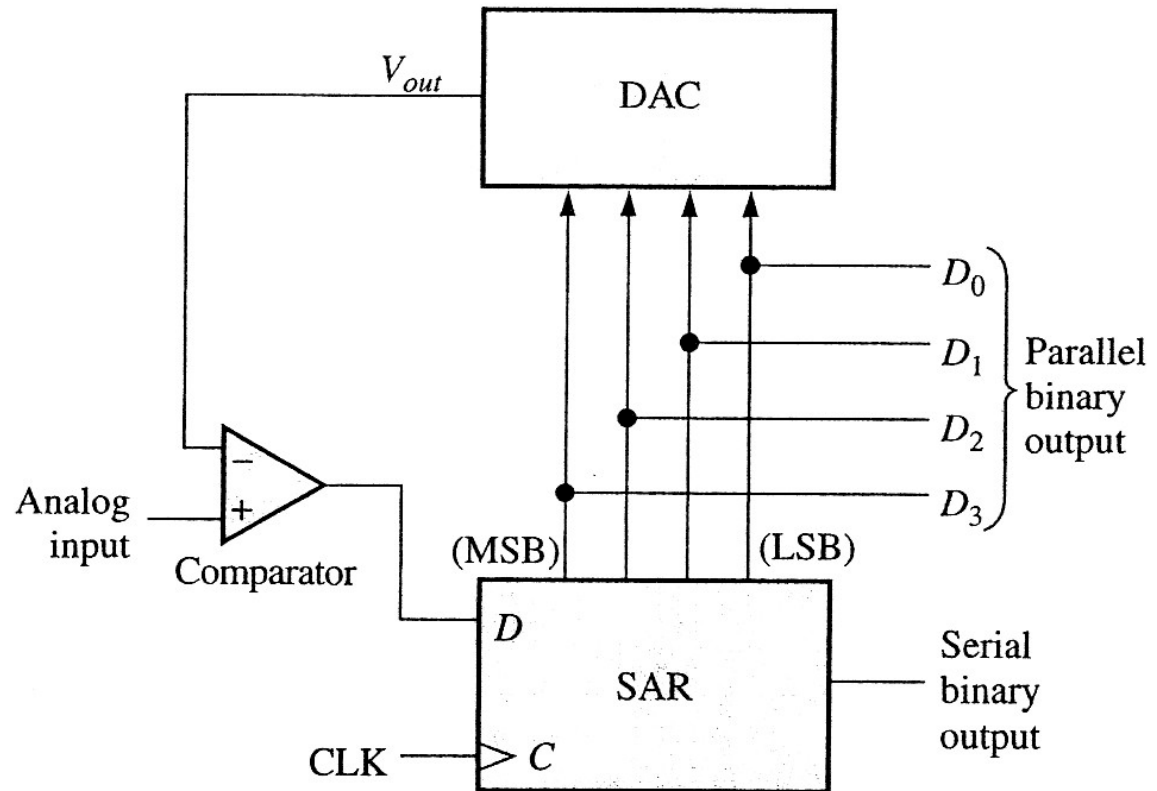
1. Essential part of many A/D converters - e.g. SAC



2. Digital waveform generators.

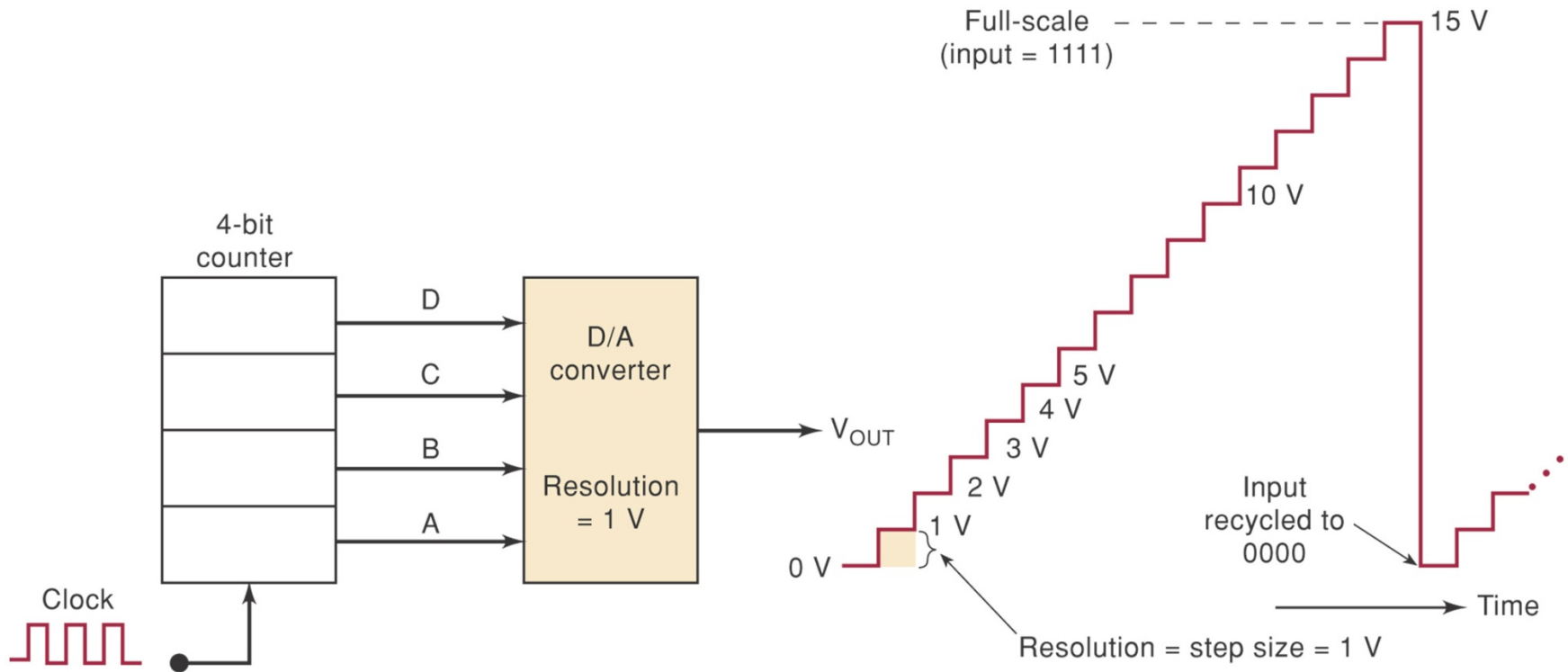

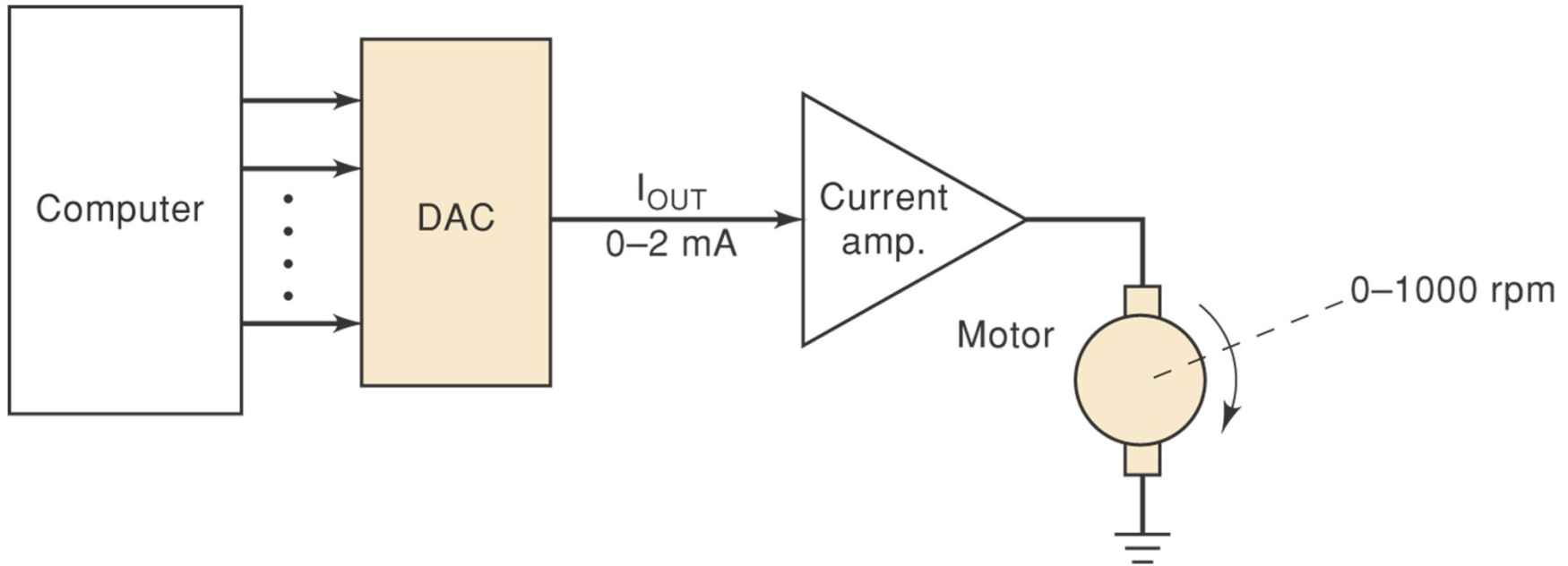3. Control current/voltage output to drive a transducer or process.




A computer controlling the speed of a motor. The 0- to 2-mA analog current from the DAC is amplified to produce motor speeds from 0 to 1000 rpm (revolutions per minute). How many bits should be used if the computer is to be able to produce a motor speed that is within 2 rpm of the desired speed?

Using nine bits, how close to 326 rpm can the motor speed be adjusted?

Basic Construction of a Digital to Analog Converter

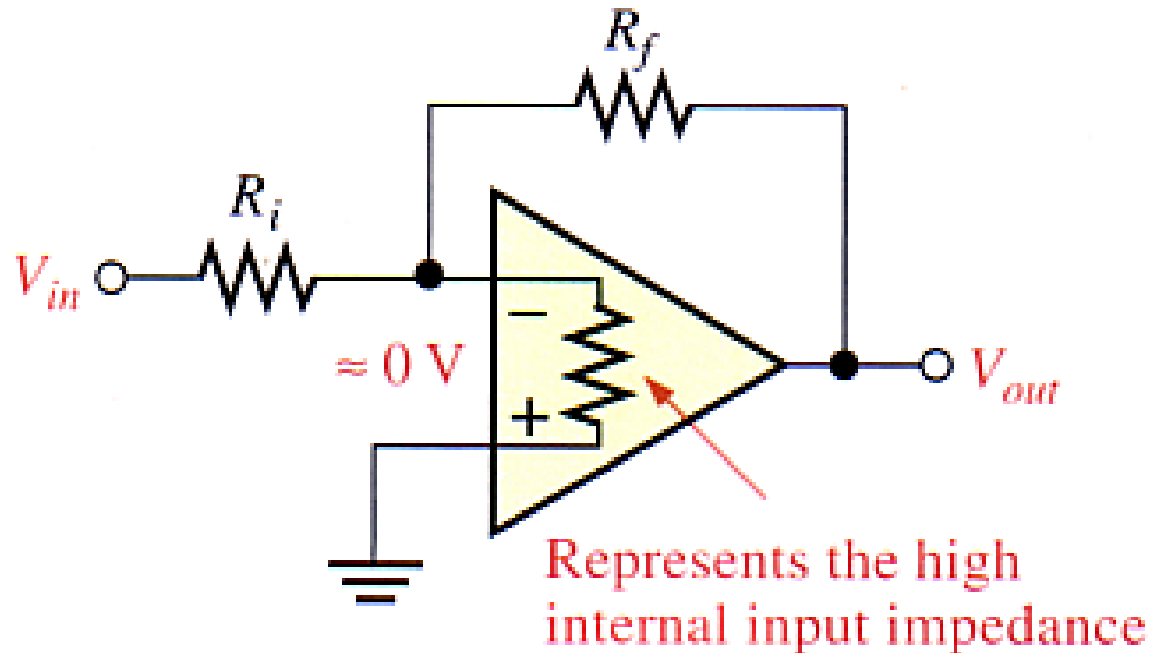
Consider the Op-amp as an inverting amplifier:



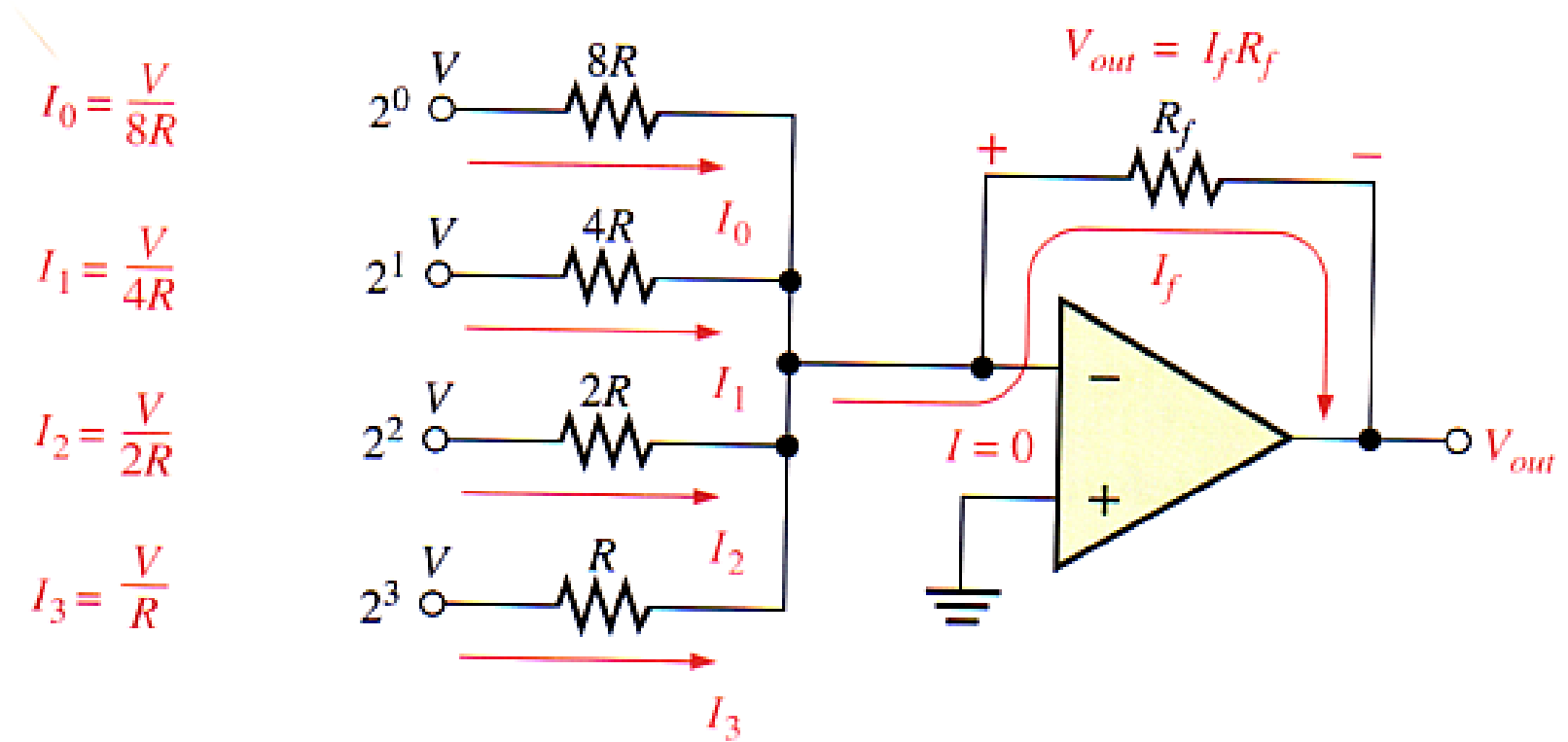(b) Op-amp as an inverting amplifier
with gain of R_f/R_i

$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$


A binary weighted input D/A converter circuit



$$V_{out} = I_f R_f = \left(\frac{V}{8R} + \frac{V}{4R} + \frac{V}{2R} + \frac{V}{R} \right) R_f$$

D/A Converter Circuitry

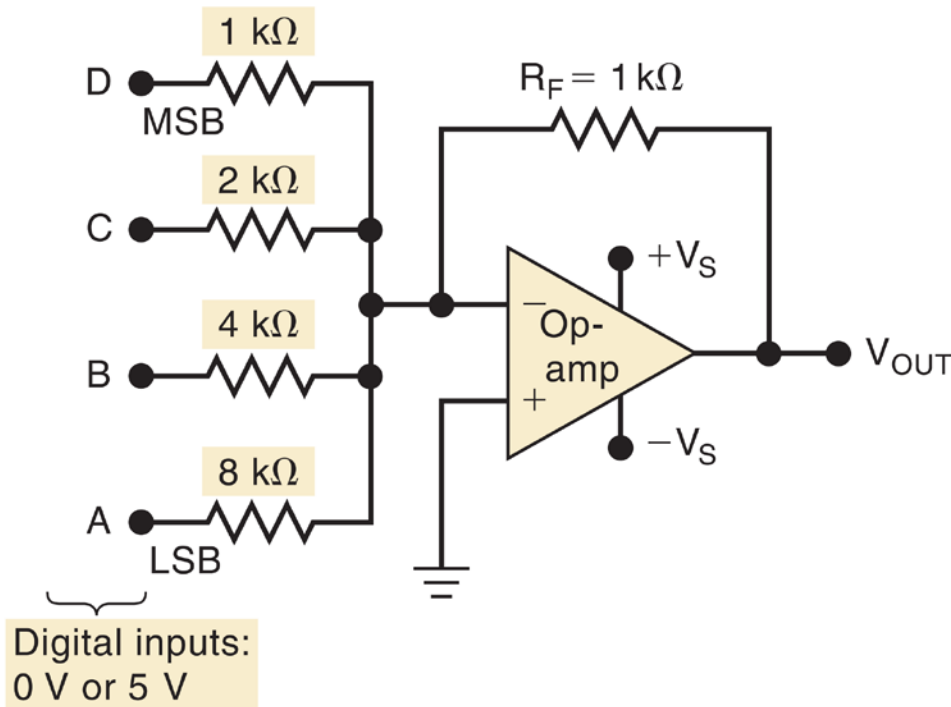- A summing operational amplifier with a resolution of .625 V




Input code				V_{OUT} (volts)
D	C	B	A	
0	0	0	0	0
0	0	0	1	-0.625 ← LSB
0	0	1	0	-1.250
0	0	1	1	-1.875
0	1	0	0	-2.500
0	1	0	1	-3.125
0	1	1	0	-3.750
0	1	1	1	-4.375
1	0	0	0	-5.000
1	0	0	1	-5.625
1	0	1	0	-6.250
1	0	1	1	-6.875
1	1	0	0	-7.500
1	1	0	1	-8.125
1	1	1	0	-8.750
1	1	1	1	-9.375 ← Full-scale

Binary Weighted DAC Example

- Example: For the binary-weighted resistor DAC below find the output when the input word is 1101_2
 $V = 10 \text{ Vdc}$, $R_f = R$

$n=4$

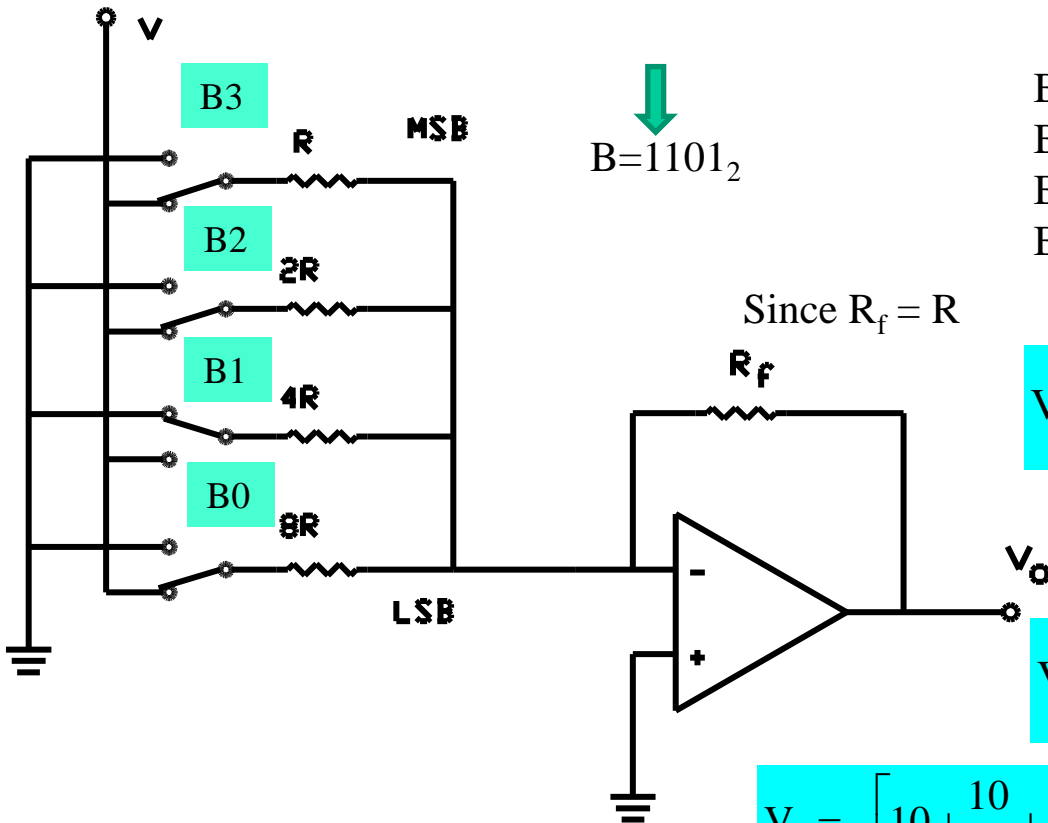

$B3=1$ MSB

$B2=1$

$B1=0$

$B0=1$ LSB

$$V_o = -R \cdot \left[\frac{B3 \cdot V}{2^{1-1}R} + \frac{B2 \cdot V}{2^{2-1}R} + \frac{B1 \cdot V}{2^{3-1}R} + \frac{B0 \cdot V}{2^{4-1}R} \right]$$

$$V_o = -\frac{R}{R} \cdot \left[\frac{1 \cdot V}{2^0} + \frac{1 \cdot V}{2^1} + \frac{0 \cdot V}{2^2} + \frac{1 \cdot V}{2^3} \right]$$

$$V_o = -1 \cdot \left[\frac{1 \cdot 10}{2^0} + \frac{1 \cdot 10}{2^1} + \frac{0 \cdot 10}{2^2} + \frac{1 \cdot 10}{2^3} \right]$$


$$V_o = -\left[10 + \frac{10}{2} + 0 + \frac{10}{8} \right] = -[10 + 5 + 1.25] = -16.25$$

Precision of the O/P voltage depends on:

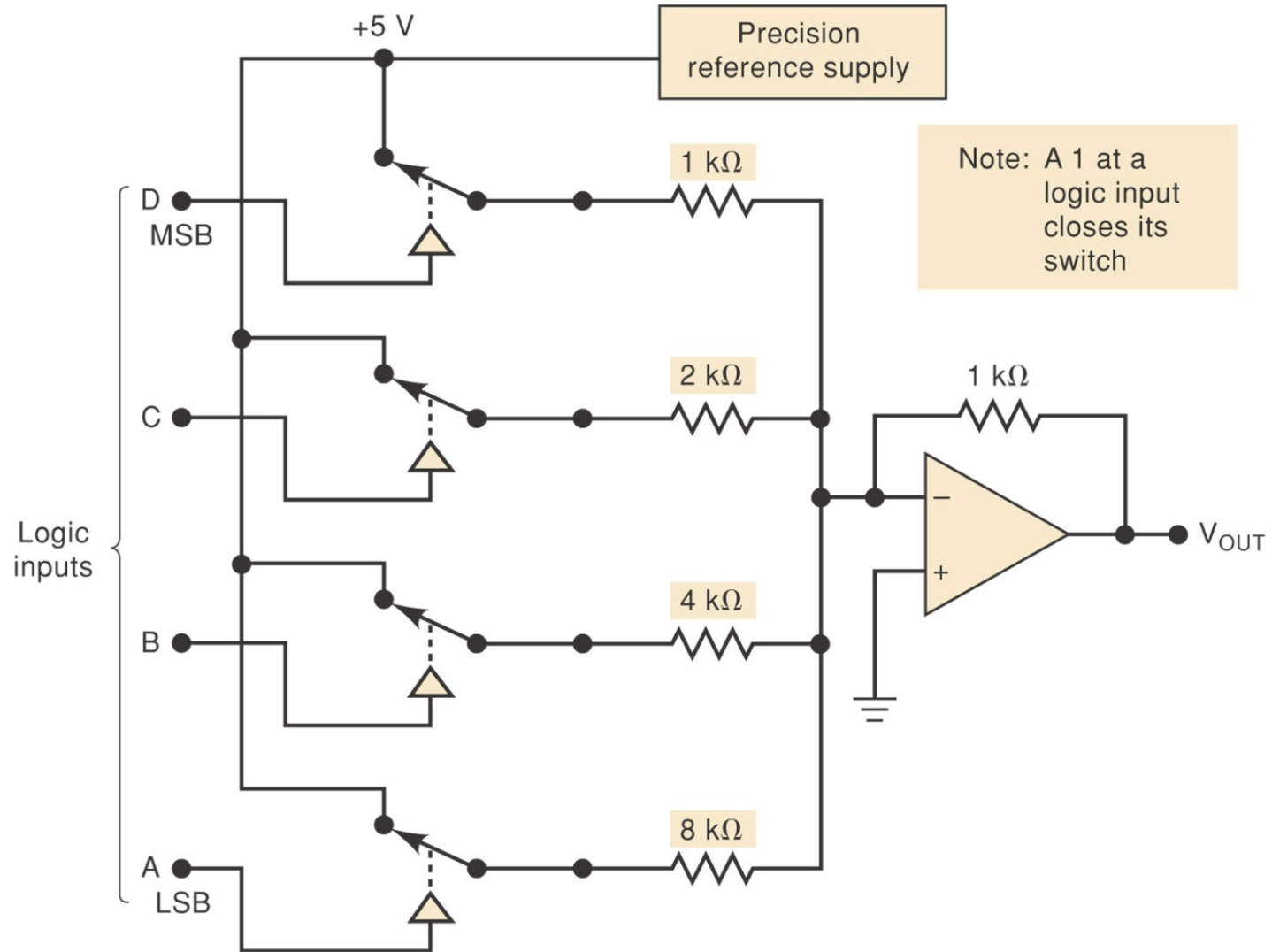
- 1) Precision of the resistors - can be made very accurate by trimming (But wide range needed !)
- 2) Precision of the I/P voltages. Need better precision than typical digital voltages. Use digital signals to select a precision voltage supply

Need additional circuitry


Complete four-bit DAC including a precision reference supply.



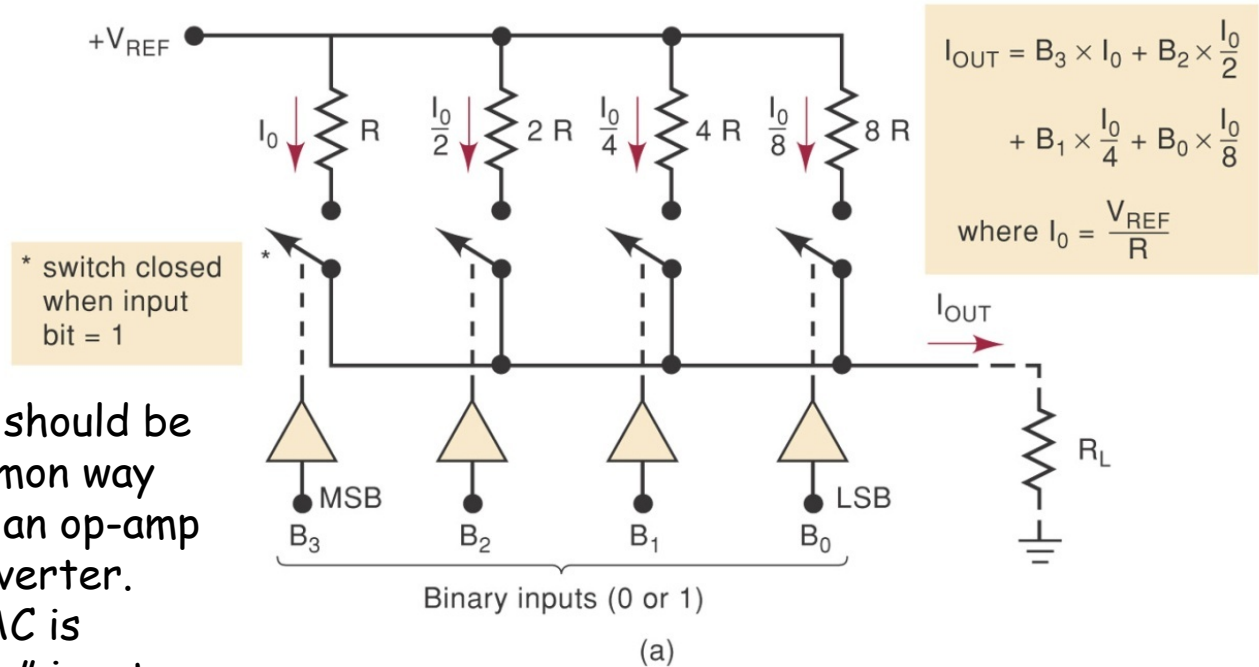(a) Basic current-output DAC; (b) connected to an op-amp current-to-voltage converter.



For I_{OUT} to be accurate, R_L should be a short to ground. One common way to accomplish this is to use an op-amp as a current-to-voltage converter. Here, the I_{OUT} from the DAC is connected to the op-amp's "-" input, which is *virtually at ground*. The op-amp negative feedback forces a current equal to I_{OUT} to flow through R_F to produce $V_{OUT} = -I_{OUT} \times R_F$. Thus, V_{OUT} will be an analog voltage that is proportional to the binary input to the DAC. This analog output can drive a wide range of loads without being loaded down.

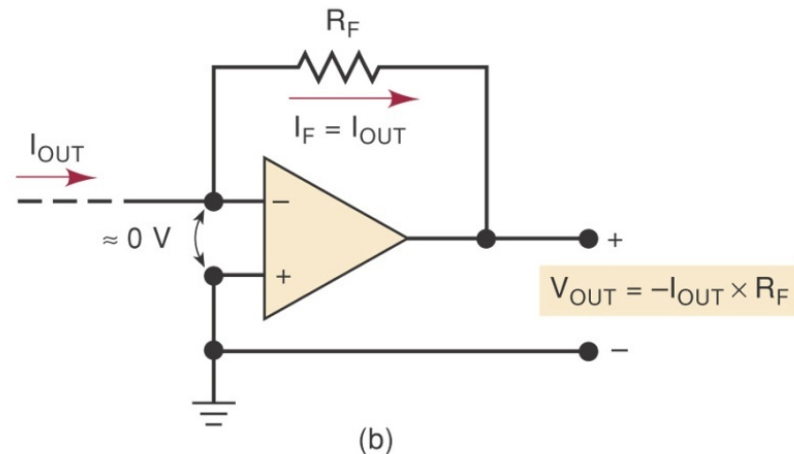

Problem 1: Assume that $V_{REF} = 10 \text{ V}$ and $R = 10 \text{ k}\Omega$
Determine the resolution and the full-scale output for this
DAC. Assume that R_L is much smaller than R .

Problem 1: Assume that $V_{REF} = 10 \text{ V}$ and $R = 10 \text{ k}\Omega$
Determine the resolution and the full-scale output for this DAC. Assume that R_L is much smaller than R .

Solution: $I_0 = V_{REF} / R = 1 \text{ mA}$. This is the weight of the MSB. The other three currents will be 0.5, 0.25, and 0.125 mA. The LSB is 0.125 mA, which is also the resolution.

The full-scale output will occur when the binary inputs are all HIGH so that each current switch is closed and

$$I_{OUT} = 1 + 0.5 + 0.25 + 0.125 = 1.875 \text{ mA}$$

Note that the output current is proportional to V_{REF} . If V_{REF} is increased or decreased, the resolution and the full-scale output will change proportionally.