

## SAMPLE TEST QUESTIONS - ANSWERS

1. Using 9-bit binary plus a sign bit, the base-10 number +338 is represented by:

(a) 1011010010

(b) 0101010010

(c) 0011010011

(d) 1011001001

S	256	128	64	32	16	8	4	2	1
0	1	0	1	0	1	0	0	1	0

2. Using 7-bit binary plus a sign bit, the 1's complement representation of the binary for -73 is:

(a) 00110110

(b) 10110101

(c) 10110111

(d) 10110110

S	64	32	16	8	4	2	1	
1	1	0	0	1	0	0	1	binary
1	0	1	1	0	1	1	0	1's comp


3. The logic gate combination on the right represents the Boolean expression:

(a)  $\overline{(A \cdot B) + C}$

(b)  $\overline{A \cdot (B + C)}$

(c)  $(A \cdot B) \oplus C$

(d)  $A \cdot (B \oplus C)$

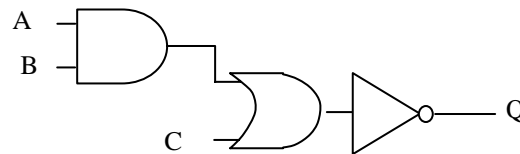

4. Select the truth table which corresponds to the Boolean expression  $\overline{(A + B)}$  ∴

(a)

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

(b)

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

(c)

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

(d)

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

5. Use 2's complement addition, representing numbers with 7-bits plus a sign bit, to perform the subtraction 76 - 119.

	<u>S</u>	<u>64</u>	<u>32</u>	<u>16</u>	<u>8</u>	<u>4</u>	<u>2</u>	<u>1</u>
+76 in binary	0	1	0	0	1	1	0	0
- 119 in binary	1	1	1	1	0	1	1	1
- 119 in 1's comp	1	0	0	0	1	0	0	0
- 119 in 2's comp	1	0	0	0	1	0	0	1

So sum is:

$$\begin{array}{r}
 01001100 \\
 + 10001001 \\
 \hline
 11010101
 \end{array}$$


Sign bit is 1 so : (i) answer is negative

(ii) answer is in 2's comp

2's comp	1	1	0	1	0	1	0	1
1's comp	1	1	0	1	0	1	0	0
binary	1	0	1	0	1	0	1	1

This is:  $-(32 + 8 + 2 + 1) = -43$

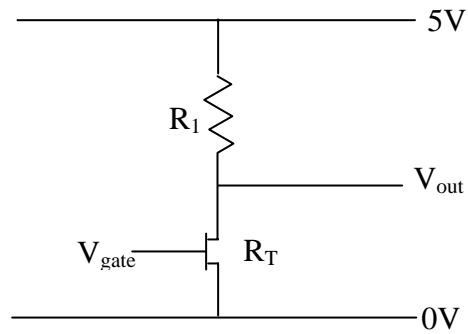6. The diagram on the right illustrates the use of a transistor as a switch in an electrical circuit (i.e. the use of the gate voltage  $V_{gate}$  applied to the transistor to control the output voltage  $V_{out}$ . Explain briefly how this is done and why using a transistor as a switch is preferable to having a mechanical switch.



**When a HIGH voltage is applied to the gate terminal of a MOSFET transistor the resistance across the transistor ( $R_T$ ) is small. When a LOW voltage is applied to the gate  $R_T$  is very large.**


**$R_1$  and  $R_T$  act as a potential divider.**

**If  $R_1 \gg R_T$  then the voltage across  $R_1$  is much larger than that across  $R_T$ . As the total voltage across  $R_1$  and  $R_T$  combined is 5 V, this means that  $V_{out}$  (voltage across  $R_T$ )  $\approx 0$  V.**

**If  $R_1 \ll R_T$  then the voltage across  $R_1$  is much less than that across  $R_T$ . This means that  $V_{out} \approx 5$  V.**

**Thus making  $V_{gate} = \text{HIGH}$  makes  $V_{out} = \text{LOW}$  and when  $V_{gate} = \text{LOW}$ ,  $V_{out} = \text{HIGH}$ .**

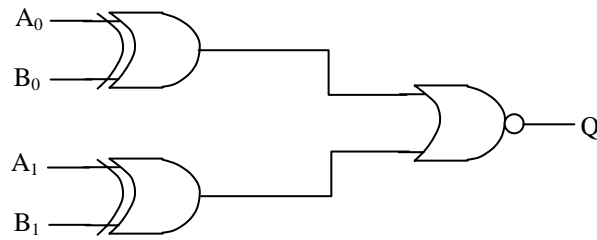7. Explain briefly the operation of the combinational logic circuit shown below.



**The top XOR gate has an output of 1 if  $A_0 \neq B_0$ .**

**The lower XOR gate has an output of 1 if  $A_1 \neq B_1$ .**

**The NOR gate will have an output of 1 only if the outputs of both the XOR gates are 0.**

**Thus Q will be 1 ONLY if  $A_0 = B_0$  and  $A_1 = B_1$ .**


**Thus the circuit tests for  $A_0 = B_0$  AND  $A_1 = B_1$ .**

8. Design a logic circuit whose output is HIGH whenever A and B are both HIGH as long as C and D are either both HIGH or both LOW.

**A gate that gives a 1 when only both its inputs are 1 is and AND gate.**

**A gate that gives a 1 when either both inputs are 1 or both inputs are 0 is an XNOR gate (XOR gate followed by a NOT gate).**

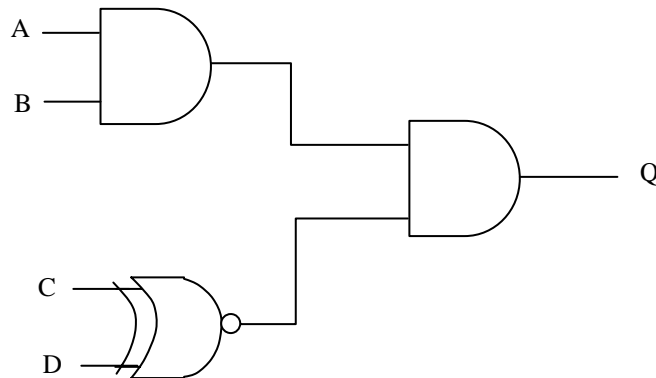**If both these conditions are to be met the outputs must go into a second AND gate.**



**In terms of Boolean algebra:  $AB(\overline{C \oplus D}) = Q$**