

EEEN203 Circuit Analysis

Transformers (Electric)

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



1

Who am I?

- Ramesh Rayudu – BEng (India), ME (Canterbury), PhD (Canterbury)
- 15 years in NZ Electricity Industry
- 13 years in NZ Academia
- Research Interests:
 - Power System Engineering – AC, DC, Renewable Energy Engineering
 - Power Electronics
 - Geothermal Energy
 - Electricity – Hydrogen Nexus

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



2

Transformers and Electricity


- Video of a transformer fault in USA
- Transformer faults are much more dangerous than any other power system faults
- Transformer blowouts cost millions of dollars (equipment and loss of power)
- At least 3 to 4 blowouts in NZ every year.



3

Transformers – the AC vs DC debate

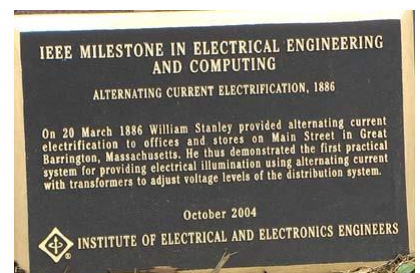- Transformers made AC usage more preferable.
- How? – by stepping up the voltage and thereby saving copper (metal)
- In non Power Electronics world (pre-1980s), they provided lower voltages for toys (non-lethal)
- Automatically regulate voltages in power systems
- A best way to match load to a source
- Highly efficient – over 95%



4

In this week?

- Look at ideal transformer first - 100% efficient
- Then we will model a real transformer
- Finally, we will include a transformer in a power system and analyse
- Why is this topic first?
 - To complete the lab next week
 - We will go through the basics of AC in week 11 and 12

5




6


Transformers

Transformers carry a lot of electricity so you must never play near or on them.


Transformers can look like this...




... or this...



... or this...






... or this...




Service pillars/pits

Service pillars are also common. They connect customers to Vector's underground cables in the street. This is what they look like.


Dangerous Voltages




Vector's Schools Programme

7

How do they run our world?

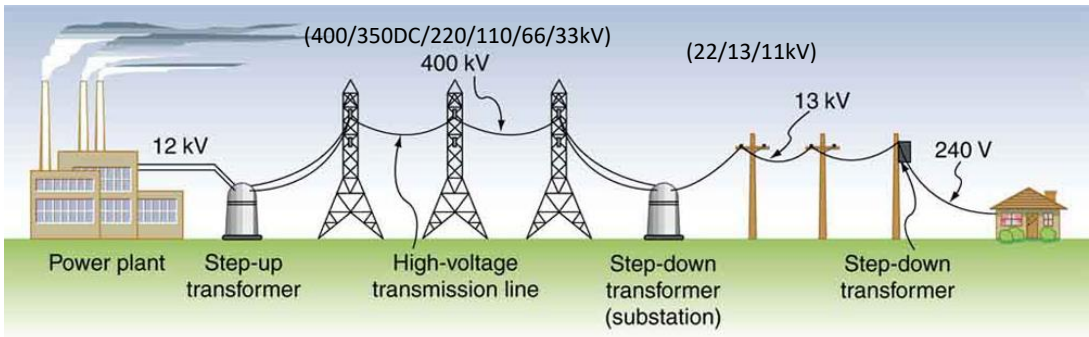


**CAPITAL THINKING.
GLOBALLY MINDED.**
MAI I TE IHO KITE PAE



8

Ideal Transformers

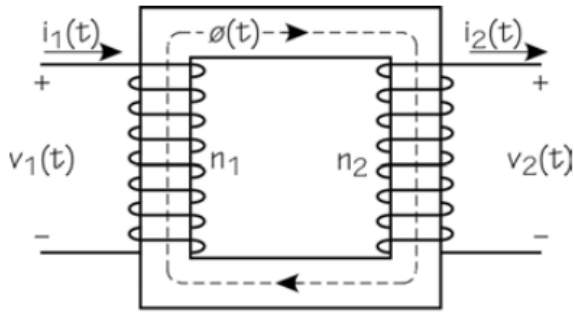

- Wrap a couple of wires around an iron core, you have a transformer – that simple
 - Electromagnetic induction or mutual induction
- Power transfer – left is primary, right is secondary; from primary to secondary
- Power transfer depends on the number of coils – basically the turns ratio of the two coils

9

How does Transformers work?

- More magnetics in EEEN313
- Faraday's laws


$$v(t) = \frac{d\phi(t)}{dt}$$

- Now use this for our transformer

$$v_1(t) = n_1 \frac{d\phi(t)}{dt}$$

$$v_2(t) = n_2 \frac{d\phi(t)}{dt}$$
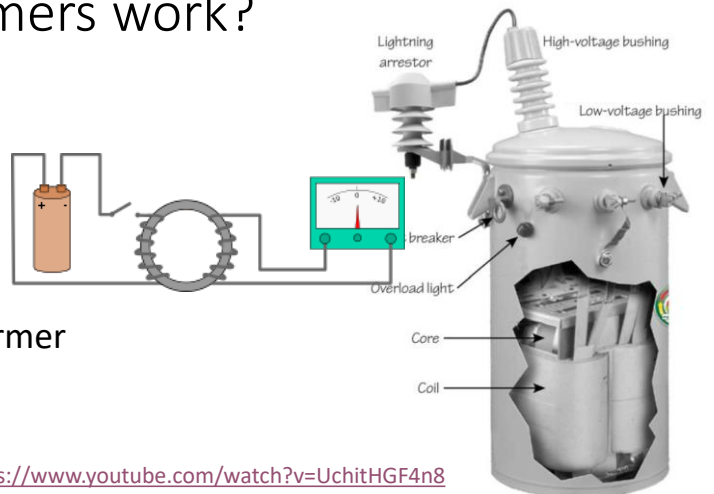
<https://www.youtube.com/watch?v=UchitHGF4n8>



10


Transformers

- Since we don't have current in the previous equation, lets use Ampere's law

$$\phi(t) \propto n_1 i_1(t)$$

$$\phi(t) \propto n_2 i_2(t)$$

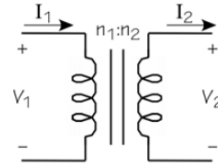- Since we use AC, we need to change to phasor notation



- Makes it easy for us to deduce simple relationships

Transformer Equations in Phasor Domain

- From Faraday's laws, we get voltage and turns ratio

$$\frac{V_1}{V_2} = \frac{n_1}{n_2}$$

- From Ampere's law, we get current and turns ratio

$$\frac{I_1}{I_2} = \frac{n_2}{n_1}$$

Impedance


- Suppose we connect an impedance to the load

$$Z_2 = \frac{V_2}{I_2}$$


- Replace V_2 and I_2 by their equivalents and we get

$$Z_2 = \frac{\frac{n_2}{n_1} V_1}{\frac{n_2}{n_1} I_1} = \left(\frac{n_2}{n_1}\right)^2 \frac{V_1}{I_1} = \left(\frac{n_2}{n_1}\right)^2 Z_1$$
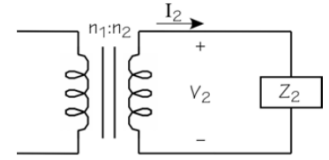
$$Z_1 = \left(\frac{n_1}{n_2}\right)^2 Z_2$$



An Example

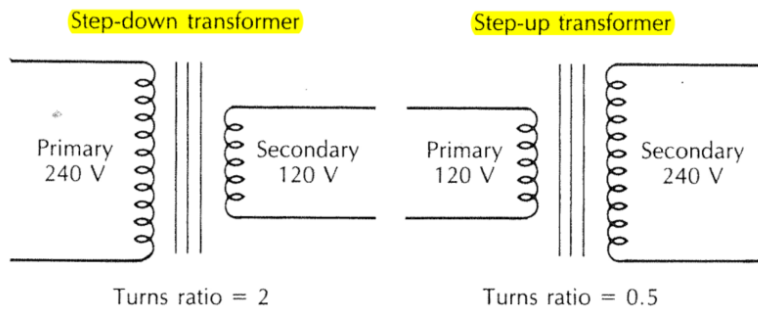

Example 2

- A step-down transformer has a turns ratio of 4 to 1 or 4. If the transformer secondary voltage is 120 V, determine the primary voltage.

$$\text{Primary voltage} = 120 \text{ V} \times 4 = 480 \text{ V}$$

Ratings of a Transformer

- Transformers are rated in volt-amps (VA) or (kilo) kVA
- VA ratings are used because the rating of a transformer depends on losses and losses depend on V and I.
- Ratings mean primary and secondary are designed to withstand the VI (VA or kVA) rating.

$$\text{Full-load current} = \frac{\text{VA rating}}{\text{Voltage}}$$

Type		TH08CT-100/11FN5 UNI	
No.		11LPL525913	
Year of manufacture		2014	
Rated power		100 kVA	
No. of phases		3	
TRANSFORMER to specification IEC (IEC) 60076-1			
Rated voltage (V)		5.25	
Current (A)		1175 AC2B	
Insulation level		LV415	
HV		11000 ±2x2.5%	
LV		110/10 AC3	
Tap no. (V) voltage (V)	Connection symbol	Dyn11	
1 11550	Cooling	ONAN	
2 11275	Rated frequency	50 Hz	
3 11000	Short-circuit imp.	3.88 %	
4 10725	Load losses	1750 W	
5 10450	No-load losses	145 W	
Total mass		452 kg	
Ambient temp		40°C	
Temperature class of		Mass of active part	
		279 kg	
Winding		Mass of oil	
50N		1100 kg	
Oil		Type of oil	
		Mineral oil Type 1	
Weighting material		Oil to	
55N		IEC 60296	
Mass of winding		216 kg	
		Core material: grain-oriented electrical steel	
		Mass of core: 189 kg	


Example

- A single-phase transformer with a 2-kVA rating has a 480-V primary, and a 120-V secondary. Determine the primary and secondary full-load currents of the transformer.

Primary full-load current $= \frac{2 \text{ kVA} \times 1000}{480 \text{ V}} = 4.17 \text{ A}$
Secondary full-load current $= \frac{2 \text{ kVA} \times 1000}{120 \text{ V}} = 16.67 \text{ A}$

- Note: Transformer current will be higher in the winding that produces low voltage (saving of copper)
- Homework: Given secondary current, how do you get primary full load current?

Example 1

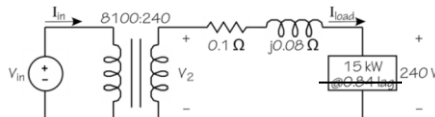

We need to supply a 15 kW load at 240V. Find the supply side voltage and current. **Assume unity power factor.**

$$I_{\text{LOAD}} = \frac{15000}{240 \times \text{PF}(1)} = 62.5 \text{ A}$$

$$V_2 = \text{load voltage} + V_{\text{drop across the } Z_{\text{line}}}$$

$$V_2 = 240 + (0.1 + j0.08) \times 62.5$$

$$V_{\text{in}} = \frac{8100}{240} \times V_2$$



$$I_{\text{in}} = \frac{240}{8100} \times I_{\text{LOAD}}$$

Power delivered by generator

$$P_{\text{in}} = |V_{\text{in}}| |I_{\text{in}}|$$

'Reflected' through transformer

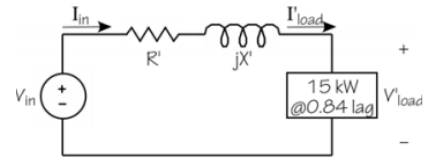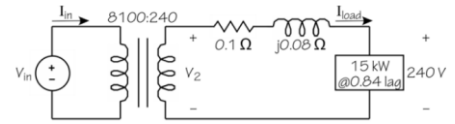- We know that voltage goes through by the turns ratio, current by the inverse of the ratio and impedance by ratio squared.
- Since power is conserved, we can 'reflect' the load through the transformer.



$$V'_{load} = \frac{8100}{240} 240 = 8100 \text{ V}$$

$$R' = \left(\frac{8100}{240}\right)^2 0.1 = 113.9 \text{ } \Omega$$

$$X' = \left(\frac{8100}{240}\right)^2 0.08 = 91.1 \text{ } \Omega$$

$$I'_{load} = \frac{15000}{(8100)(0.84)} \angle -\cos^{-1} 0.84 = 2.205 \angle -32.9^\circ \text{ A}$$

$$V_{in} = 8100 + (113.9 + j91.1) 2.205 \angle -32.9^\circ$$

$$= 8100 + 321.6 \angle 5.8^\circ = 8420 \angle 0.2^\circ \text{ V}$$

Real Transformer


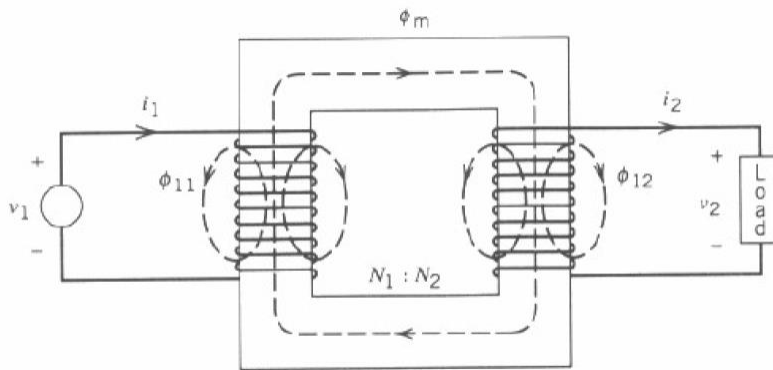
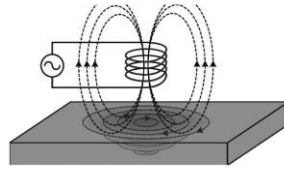
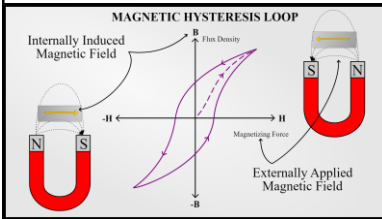


FIGURE 4.10 An actual transformer.

Real Transformers

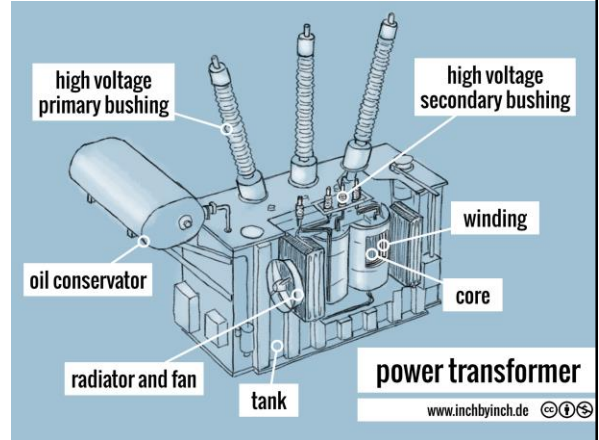- Have resistance in the windings
- Not all of the flux produced by one winding links with the other (flux leakage)
- Magnetic core has finite permeability
- Core losses
 - Hysteresis
 - Eddy currents




21

Real Transformers

- Transformers are made of wires and each wire has a resistance
- Since Transformer coils look like inductors, there would be some inductance too

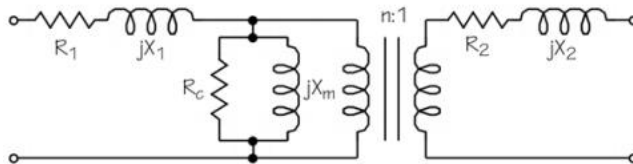
X_1 and X_2 are leakage reactance
 R_c is core loss
 X_m is magnetic reactance



22

Model with real numbers

- From a 20 kVA, 4160-240 V transformer

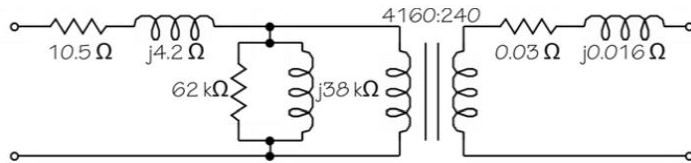

- Wire resistances are minimised; we want low core losses
- Note the series elements are small and parallel ones are large
- Moving the parallel elements to the right of series elements- less effect on the main current flowing through the series elements.

Transformer Losses

Transformer losses consist of:

- Copper losses in the windings
 - Depend on load current
- Hysteresis and eddy-current losses in the core
 - Constant for constant flux (constant voltage) conditions
- Stray losses due to currents induced by leakage fluxes in the transformer structure
 - Negligible for a well-designed transformer

The maximum total losses in a transformer account to < 3%

Transformer Rating


Transformer ratings are provided to keep the operating temperature within acceptable limits. A transformer's rating is based upon the following:

- Nominal current
 - To limit copper losses
- Nominal voltage and frequency
 - To limit core losses
 - Transformer size based upon flux density limit in core material
- Apparent power rating
 - Based on product of nominal current and nominal voltage
 - A transformer can become fully loaded at sufficient levels of reactive power, even if no real power is being delivered.
- Cooling



Transformer Cooling

- Cooling of a transformer increases the rate of heat dissipation and hence improves the transformer rating:
- Low-voltage indoor transformers (<200kVA) can be passively air-cooled via natural convection
- Relative to air, oil is a better thermal conductor and electrical insulator, so it is invariably used for cooling of high-voltage, high-power transformers.
- As power rating increases, radiators, heat exchangers and forced oil/air circulation may be added to improve power dissipation

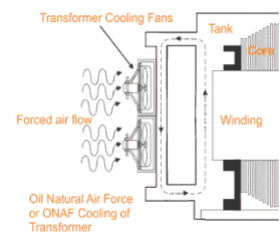

Transformer Construction

Power transformers are designed such that their characteristics approach the ideal:

- To attain high permeability, cores are made of iron-based materials
- To minimise core losses, core is laminated from high-resistivity, high-grade silicon steels
- Leakage reactances are minimised by co-winding of the coils
- Geometries are optimised to minimise turn lengths, maximise core window areas and achieve highest power densities



Types



(a)




(b)

Figure 64: E-I (a) and toroidal (b) transformers.

- E-I has E shaped steel capped with I shaped pieces
- Toroidal are built around a ring shaped core of silicon steel
 - Eliminates air gaps
 - Better than E-I in several ways
 - Can be used at higher frequencies in SMPS


Transformer Testing

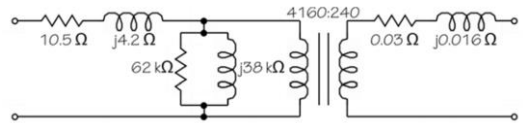- So how do we get the real transformer numbers stated before?
- Two basic transformer tests:
 - Open circuit test
 - Short circuit test
- All measure the current, voltage and power



Open-circuit test

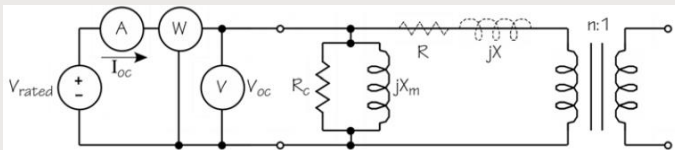- Tells us how the transformer behaves under the rated voltage
- Ammeter, Voltage and Wattmeter measure I_{oc} , V_{oc} , P_{oc}
- Note, no load connected – secondary is left open
- So the current is very less – series elements have less effect



$$P = |V||I| \cos(\theta_v - \theta_i)$$

$$\angle I_{oc} = -\cos^{-1} \frac{P_{oc}}{|V_{oc}||I_{oc}|}$$

$$I_{oc} = |I_{oc}| \angle I_{oc} = I_c - jI_m$$


We know the voltage in the parallel elements,
So we can find the impedances

The two parallel elements are:

$$R_c = \frac{|V_{oc}|}{I_c}, \quad X_m = \frac{|V_{oc}|}{I_m}$$

Short-circuit Test

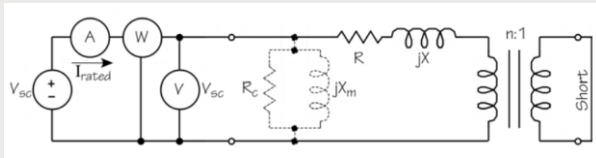- This is rated current test – so we short the secondary – wiring the terminals together.
- We apply a small voltage to the primary, just enough to drive the rated current into the transformer.
- So the parallel elements have small effect.
- Series elements carry the rated current.



Phasor Currents:

$$\angle I_{sc} = -\cos^{-1} \frac{P_{sc}}{|V_{sc}| |I_{sc}|}$$

$$I_{sc} = |I_{sc}| \angle I_{sc}$$

Impedance of series elements:

$$R + jX = \frac{|V_{sc}|}{I_{sc}}$$

Real and imaginary parts of impedance:

$$R = \operatorname{Re} \left[\frac{|V_{sc}|}{I_{sc}} \right], \quad X = \operatorname{Im} \left[\frac{|V_{sc}|}{I_{sc}} \right]$$

31

Example: Transformer Test

- Transformer is a 20-kVA, 4160:240 V
- Rated current for short-circuit test is 20 kVA/ 4160 = 4.81A
- Find the transformer parameters

$$\begin{aligned} V_{oc} &= 4160\text{V} \\ I_{oc} &= 0.155\text{A} \\ P_{oc} &= 292\text{W} \end{aligned}$$


$$\begin{aligned} V_{sc} &= 121\text{V} \\ I_{sc} &= 4.81\text{A} \\ P_{sc} &= 509\text{W} \end{aligned}$$

We will revisit this after our lectures on 'Power' this week.

32

Load at Unity Power Factor - Example

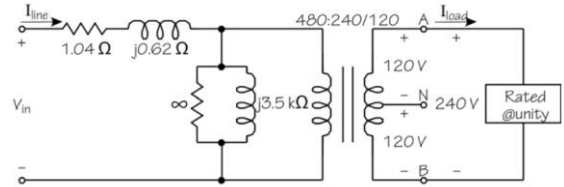A 10 kVA, 480:240/120 V supplies 240 V at rated load
 Unity Power Factor
 Find voltage regulation in percentage.
 Rated Load? – means we have to supply 10 kVA no
 matter what the power factor is!




- If the transformer rating is 10 kVA and it's supplying rated load, that rating is the same on both sides of the transformer.
- Therefore, I can calculate rated current on the primary side by dividing total power by the primary voltage:

$$I_{\text{rated}} = \frac{10 \times 10^3}{480} = 20.8 \text{ A}$$

$$V_{\text{in}} = 480 + (1.04 + j0.62) 20.8 \angle 0^\circ \\ = 480 + 25.2 \angle 30.8^\circ = 501.8 \angle 1.5^\circ \text{ V}$$
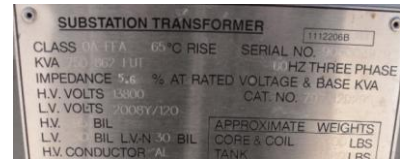
$$\%VR = 100 \frac{501.8 - 480}{480} = 4.5\% \quad \text{Good! } < 5\%$$



Load at Unity Power Factor - Example


- The only loss in the transformer is the series resistance – wire heating
- Parallel branch has only inductance; resistance is very large (ignore)
- Losses

$$P_{\text{losses}} = 1.04 \times 20.8^2 = 450 \text{ W}$$

- Efficiency $\% \eta = 100 \frac{10}{10 + 0.450} = 95.7\%$ Good Again!

- But what happens if we have a poor power factor? – very common now
- We will look at this when we discuss Power Factor

Peculiar Transformer

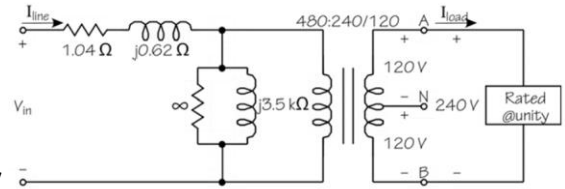

- Notice extra terminal on the secondary
- This is called center (US spelling)-tapped transformer
- This is a common configuration in USA to supply homes
- A-N or B-N is 120 V; A-B is 240 V
- Each home there has a Centre tapped Transformer; 120V supplies appliances and lights, 240 V supplies AC, water heater, kitchen range (big loads)
- Both sides on the Transformer in the lab is centre tapped (basically taking output at half the number of coils)

Summary

- Transformers are simple elements that keep our mobiles phones and game consoles on (and also working) all the time (and also transform electricity)
- Are bidirectional
- Voltage go through turns ratio; current as inverse; impedance as the square.
- Power is conserved
- Real transformer has series and parallel resistance and reactance
- Their values can be determined by open and short circuit tests